

Lab 7

Single-Cycle CPU Lab

Video Link : <https://youtu.be/1YRKz1B4Ed8>



Outline

1. Introduction
2. ISA / Verilog Review
3. CPU Architecture Review
4. Example of CPU Micro-Architecture



Pework of implementing a CPU

You need to **be familiar with** ...

- | | |
|---|----------------------------|
| 1. ISA | (Lab2 ~ Lab3 – RISC-V ISA) |
| 2. HDL (Verilog / SystemVerilog / VHDL) | (Lab4 ~ Lab6 – Verilog) |
| 3. Concept of CPU Architecture | (Lab7) |



ISA / Verilog Review



ISA (Instruction Set Architecture)

Software

```
000000000000100000000001010010011
0000000000001000000000001100010011
000000000000100101001001110010011
000000000000100110001111000010011
00000001110000111000111010110011
```

Machine Instructions

ISA

ISA is an abstraction of hardware


ISA is an implementation target

Hardware

HDL

(Verilog / SystemVerilog / VHDL)

Verilog – Combinational

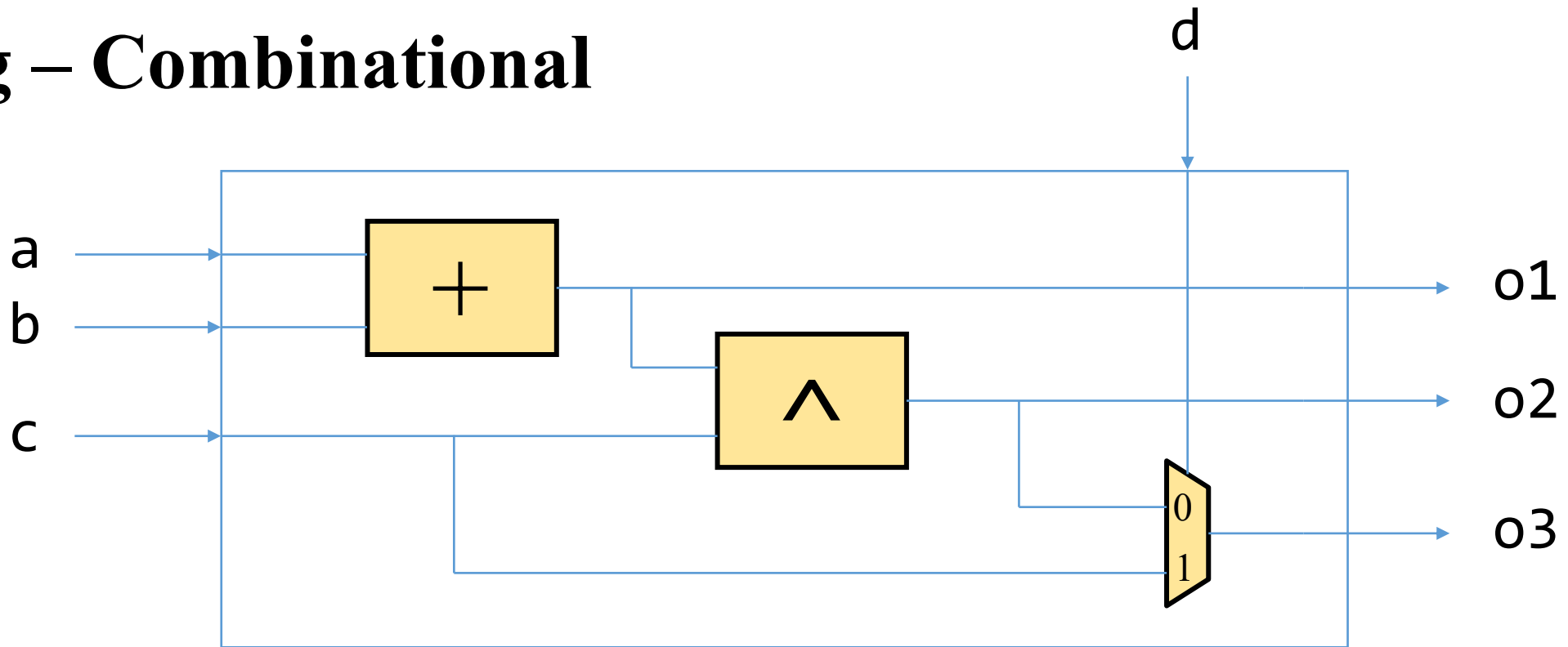

Recommand

```
wire o1, o2, o3;

assign o1 = a + b;
assign o2 = o1 ^ c;
assign o3 = (d) ? c : o2;
```

```
reg o1, o2, o3;

always @ (*) begin
    o1 = a + b;
    o2 = o1 ^ c;
    o3 = (d) ? c : o2;
end
```


```
reg o1, o2, o3;

always @ (*) begin
    o2 = o1 ^ c;
    o1 = a + b;
    o3 = (d) ? c : o2;
end
```

```
reg o1, o2, o3;

always @ (*) begin
    o1 = a + b;
    o2 = o1 ^ c;
    if (d)
        o3 = c;
    else
        o3 = o2;
end
```

Verilog – Sequential

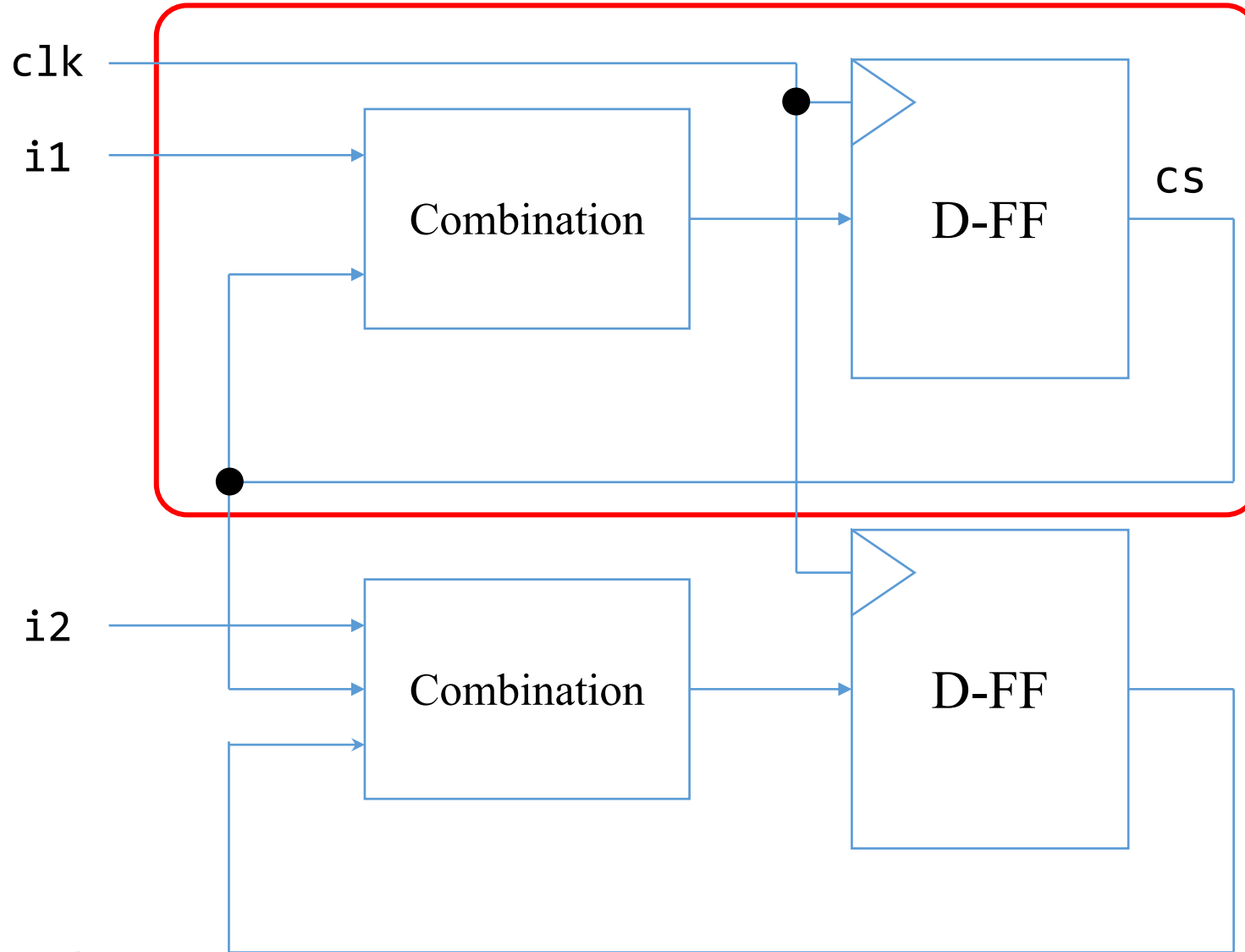


2 phases

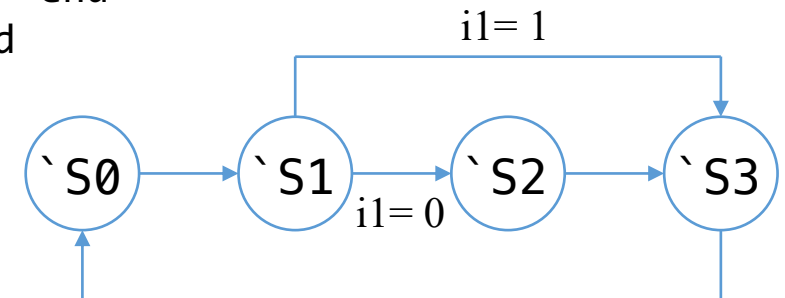
1. Evaluate (Before Clock Edge)
2. Update (When Clock Edge)

Method 1 :

```
always@(posedge clk) begin
    if (rst)
        cs <= `S0;
    else begin
        case(cs)
            `S0 : cs <= `S1;
            `S1 : cs <= (i1) ? `S3 : `S2;
            `S2 : cs <= `S3;
            `S3 : cs <= `S0;
            default : cs <= `S0;
        endcase
    end
end
```



Verilog – Sequential

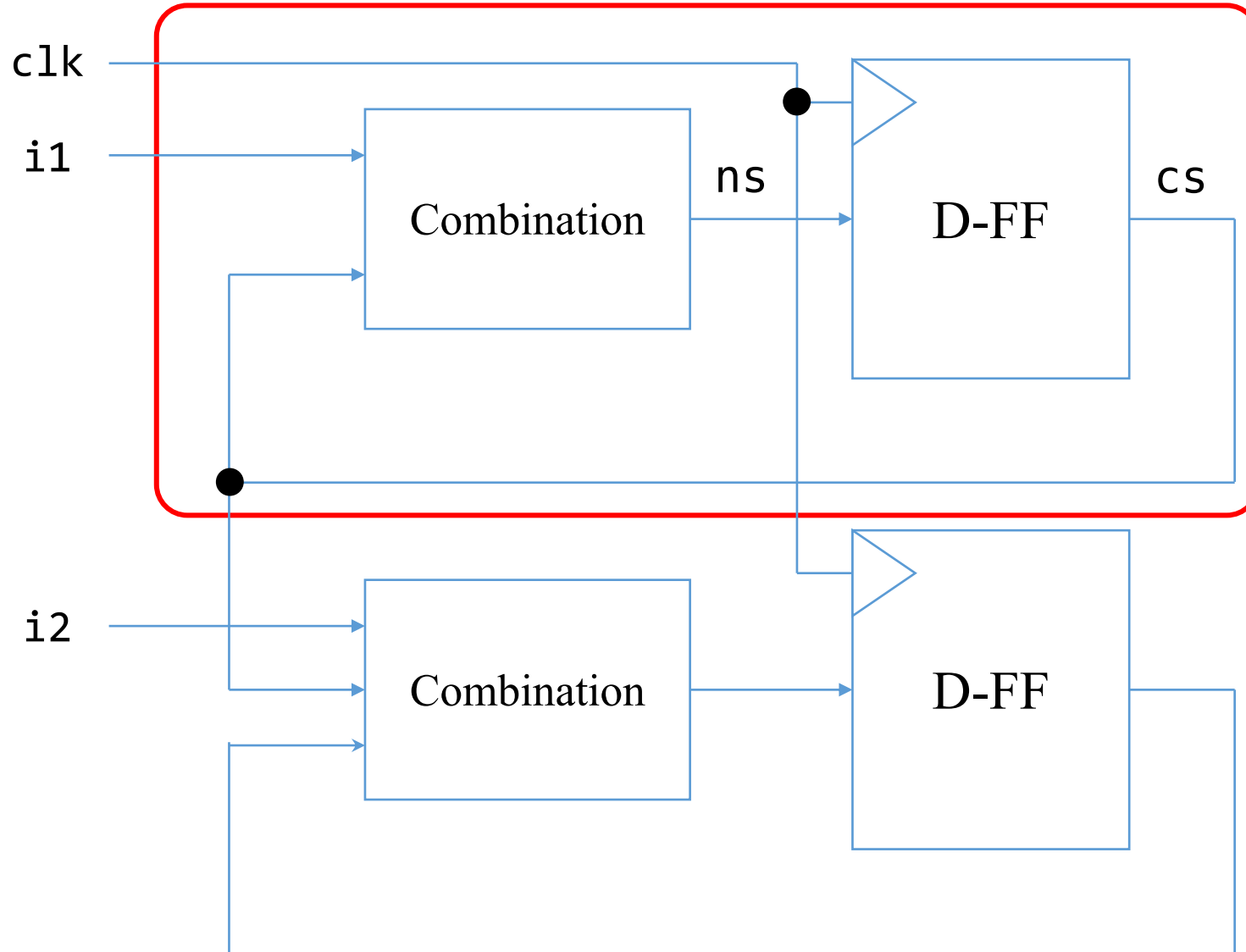

2 phases


1. Evaluate (Before Clock Edge)
2. Update (When Clock Edge)

Method 2 (Recommend) :

```
always@(posedge clk) begin
    if (rst)
        cs <= `S0;
    else
        cs <= ns;
end
```

```
always@(*) begin
    case(cs)
        `S0: ns = `S1;
        `S1: ns = (i1) ? `S3 : `S2;
        `S2: ns = `S3;
        `S3: ns = `S0;
        default : ns = `S0;
    endcase
end
```


Verilog – Sequential

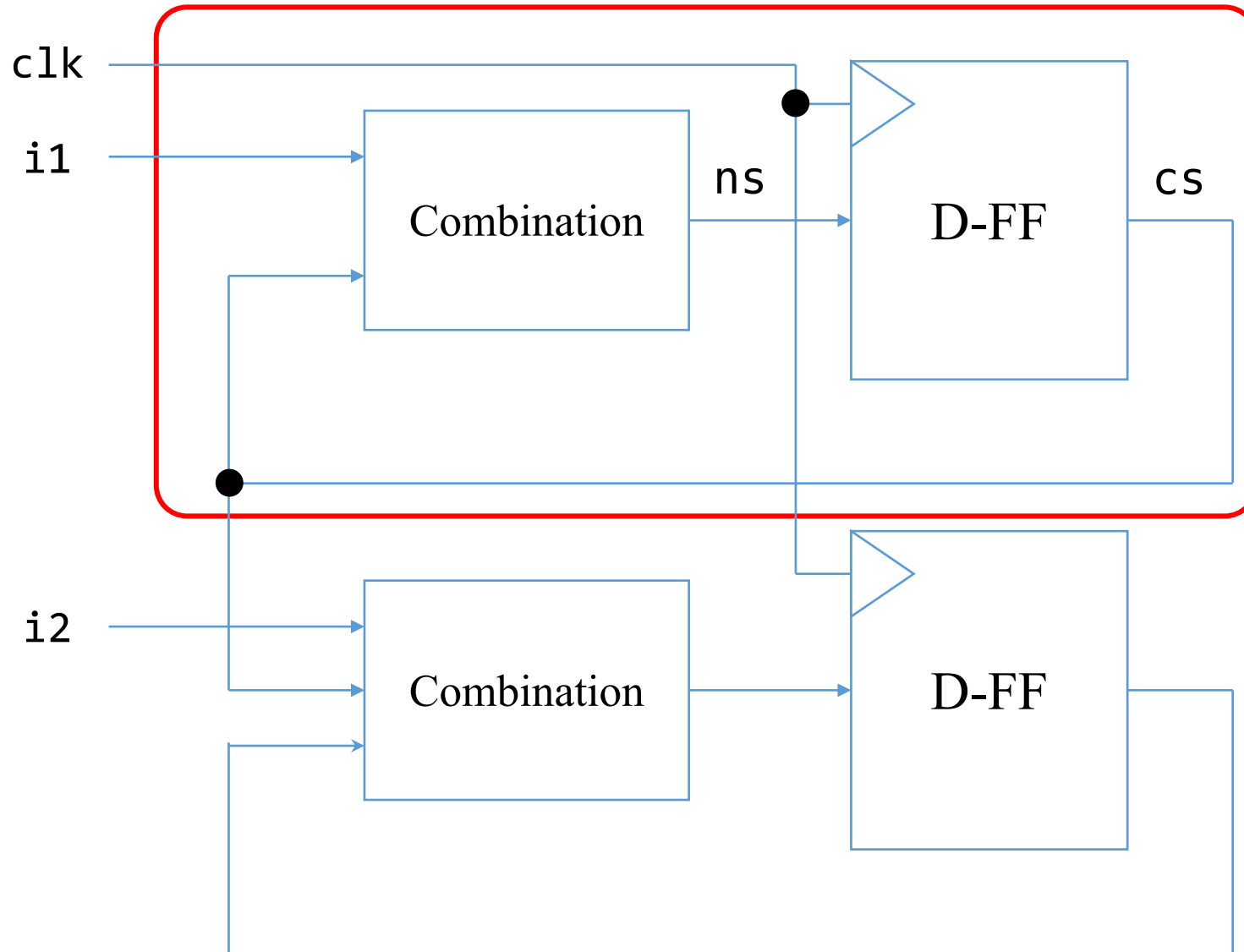

2 phases


1. Evaluate (Before Clock Edge)
2. Update (When Clock Edge)

Method 2 (Recommend) :

```
always@(posedge clk or posedge rst) begin
    if (rst) Asynchronous
        cs <= `S0;
    else
        cs <= ns;
end
```

```
always@(*) begin
    case(cs)
        `S0: ns = `S1;
        `S1: ns = (i1) ? `S3 : `S2;
        `S2: ns = `S3;
        `S3: ns = `S0;
        default : ns = `S0;
    endcase
end
```

Verilog – Sequential

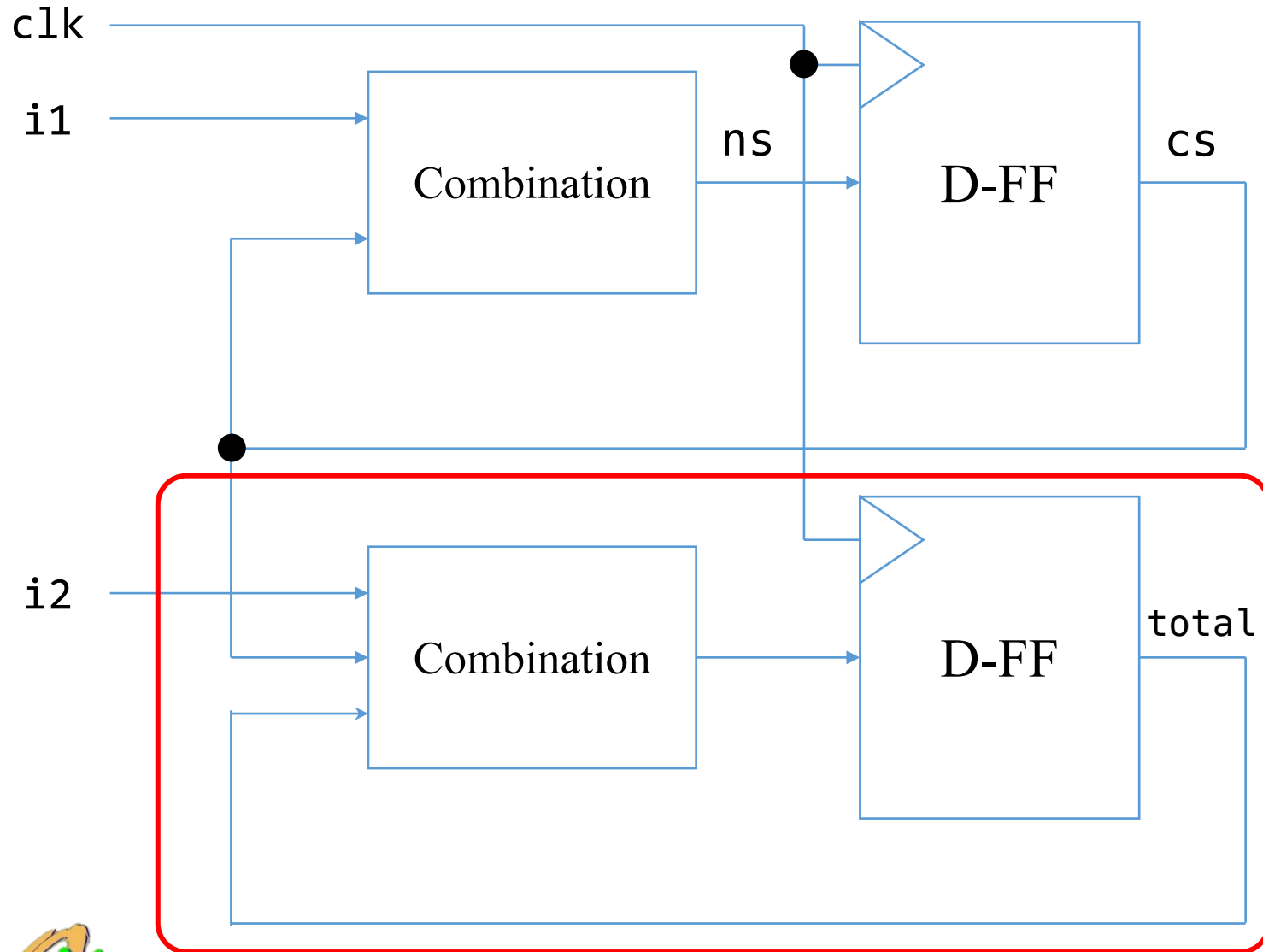


2 phases

 
1. Evaluate (Before Clock Edge)
2. Update (When Clock Edge)

Method 1 :

```
always@(posedge clk) begin
    if (rst) begin
        total <= 0;
    end
    else if (cs == `S3) begin
        total <= 0;
    end
    else begin
        total <= total + i2;
    end
end
```



Verilog – Sequential

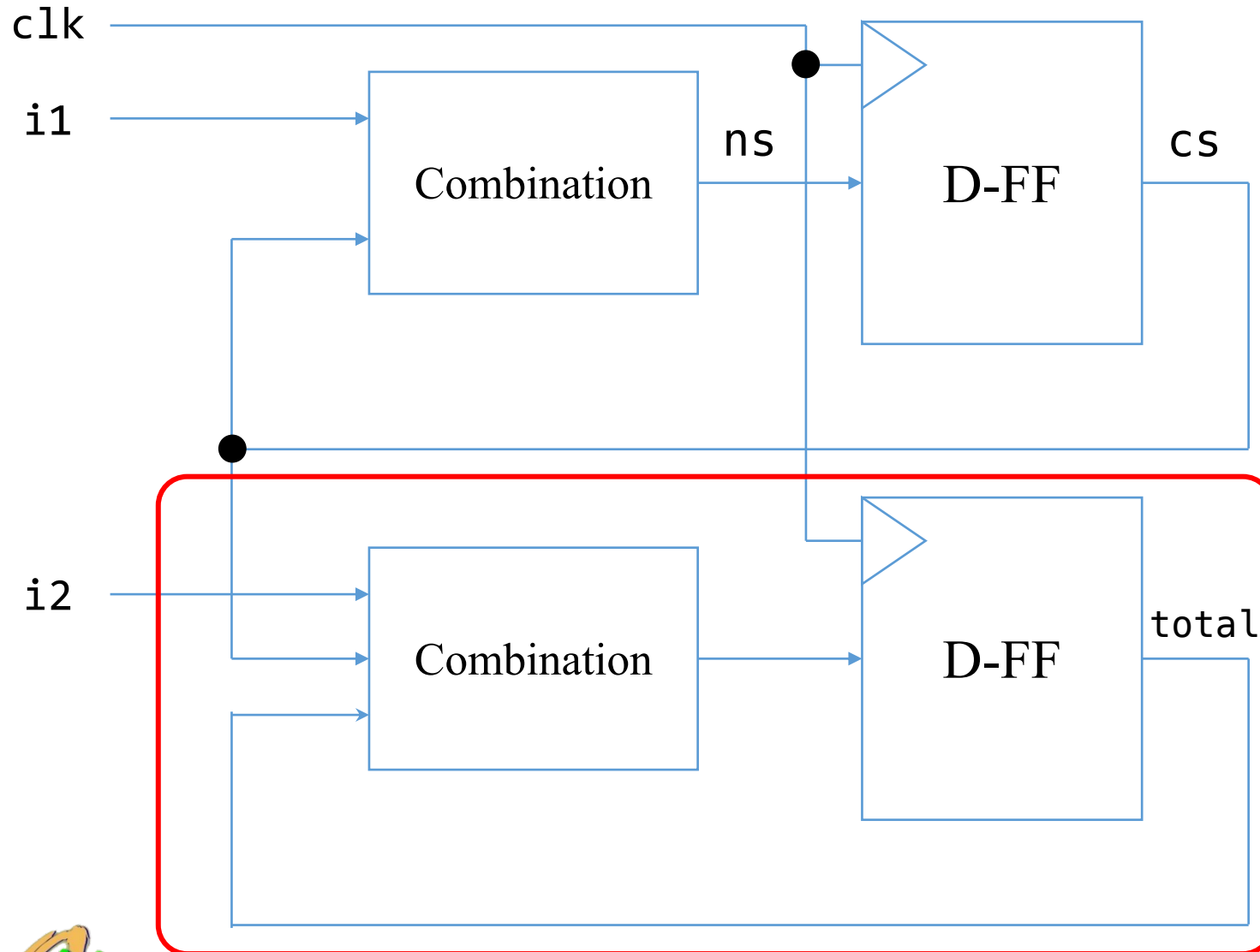

2 phases


1. Evaluate (Before Clock Edge)
2. Update (When Clock Edge)

Method 2 :

```
always@(posedge clk) begin
    if (rst) begin
        total <= 0;
    end
    else if (cs == `S3) begin
        total <= 0;
    end
    else begin
        total <= total_tmp;
    end
end

assign total_tmp = total + i2;
```


Verilog – Combinational

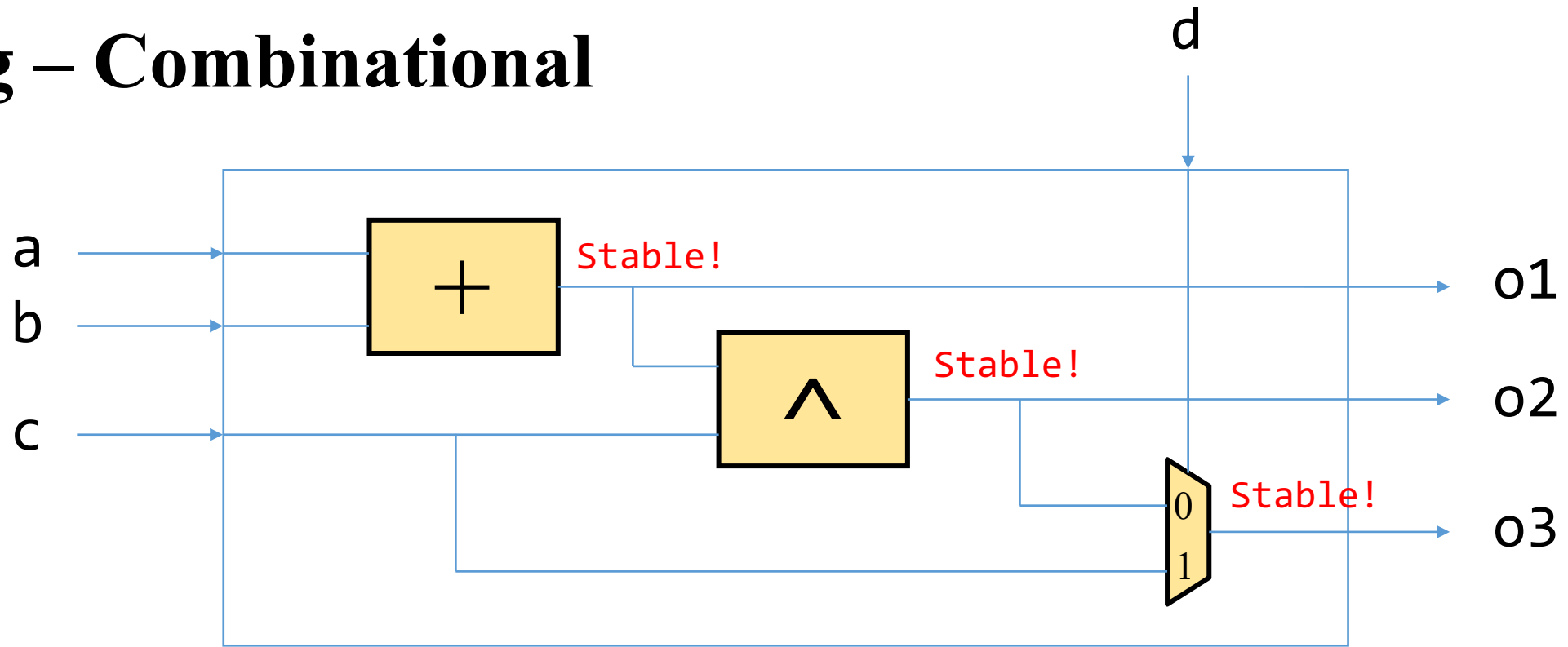


Stable!

~~Stable?~~
Stable!

Verilog – Moore v.s. Mealy

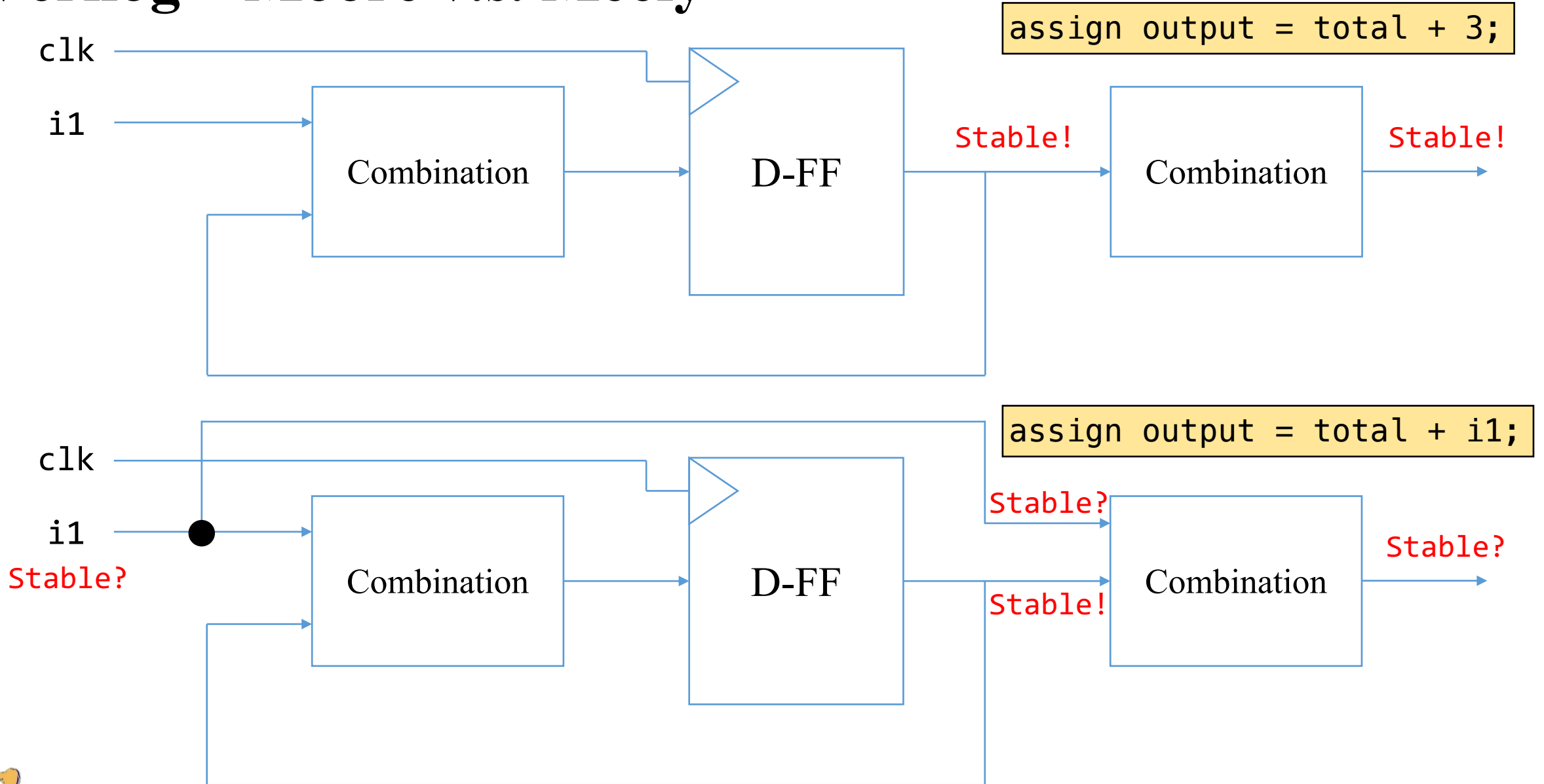

Verilog – Attention !

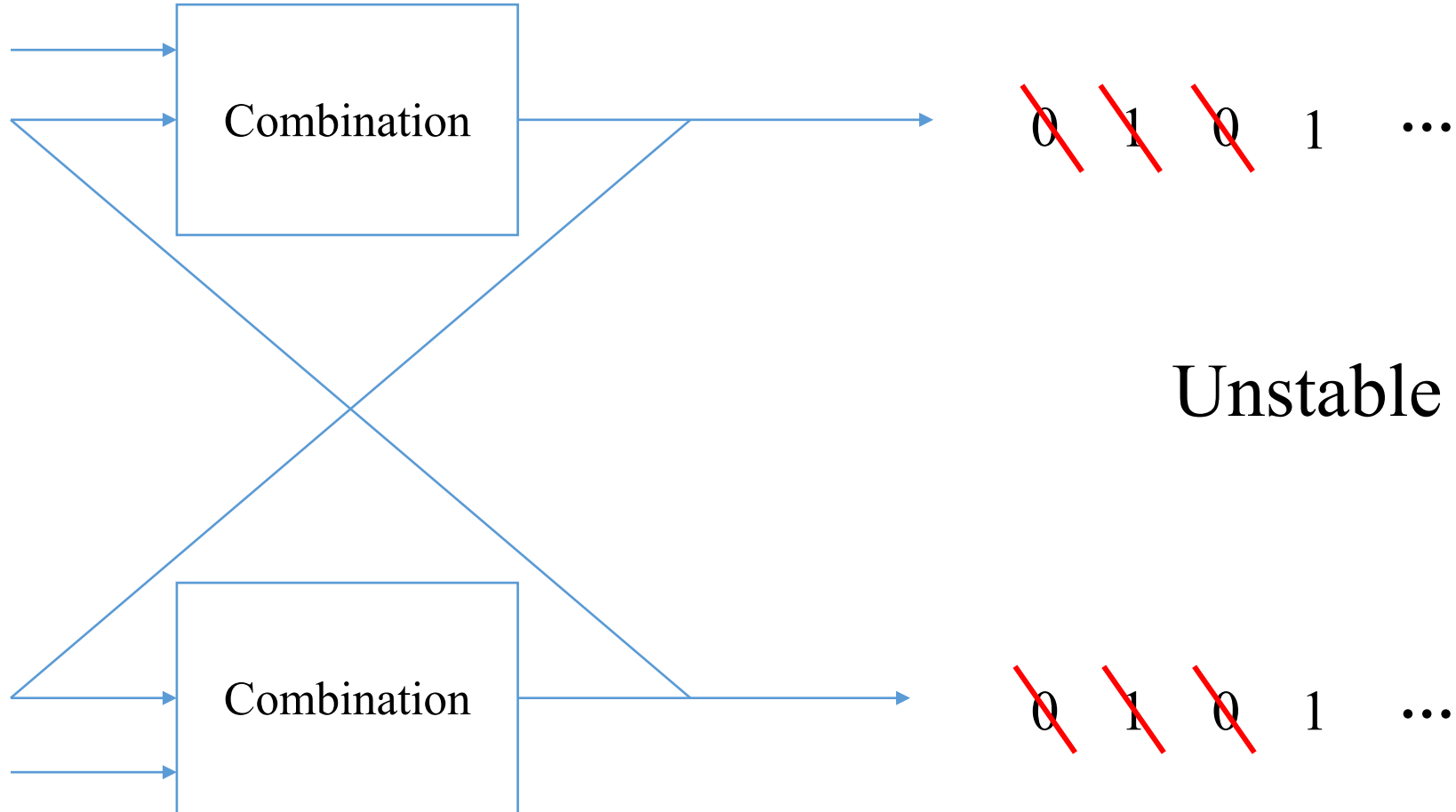


Unstable ,Oscillating Signal

Verilog – Attention !

- **Sequential circuit**

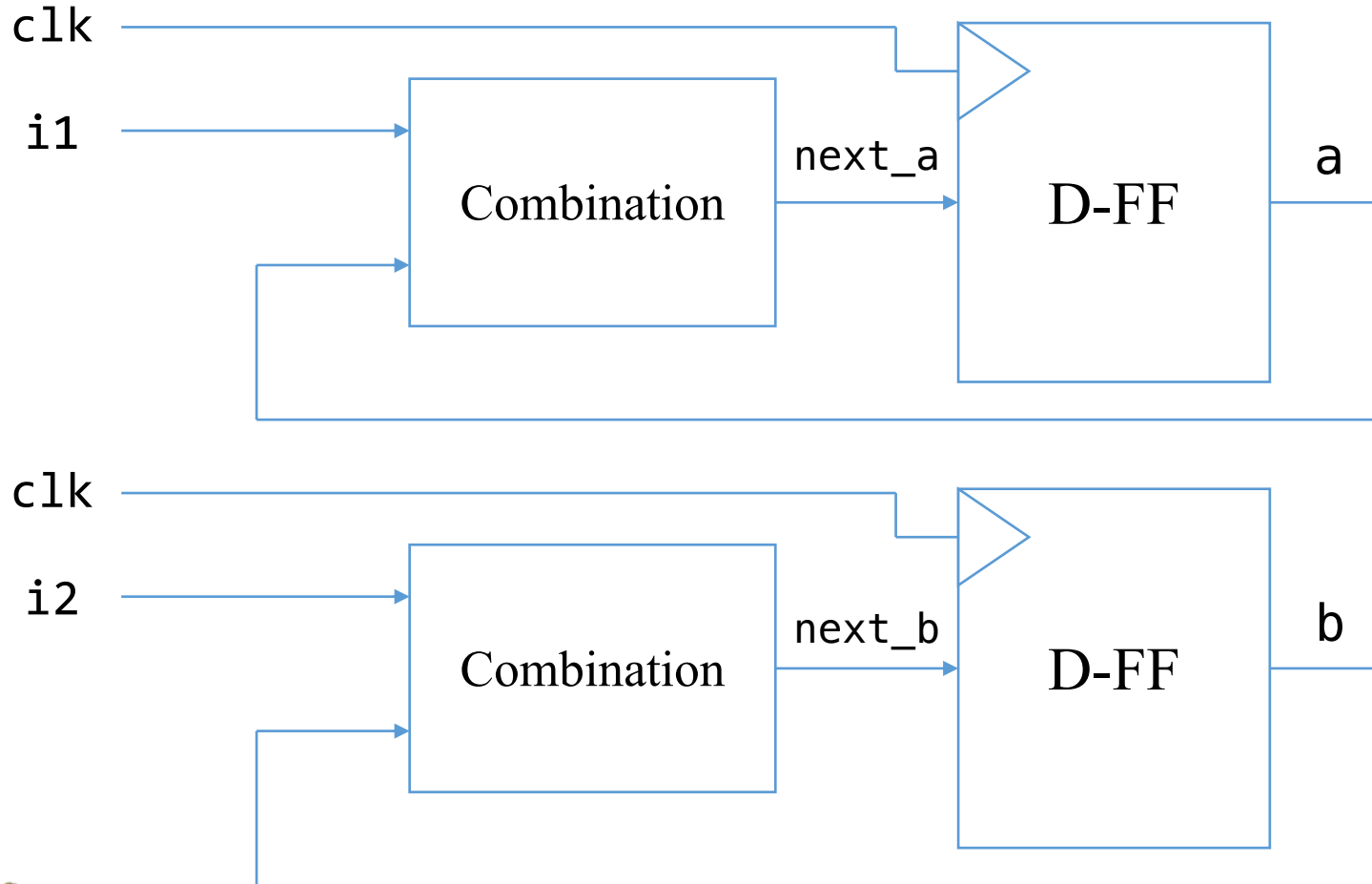always @ (posedge clk) : **Always use non-blocking assignment (<=)**





```
always@(posedge clk) begin
    if (rst) begin
        a <= 0;
        b <= 0;
    end
    else begin
        a <= next_a;
        b <= next_b;
    end
end
```

```
assign next_a = ... ;
assign next_b = ... ;
```

Verilog – Attention !

- **Combinational circuit**

  always @ (*) : **Can use blocking (=) or non-blocking (<=) , but can't mix**



Don't mix


```
always @ (*) begin
    a <= i0 + i1;
    b <= i2 + i3;
end
```

```
always @ (*) begin
    a <= i0 + i1;
    b <= i2 + i3;
    c = a + i3;
end
```

```
always @ (*) begin
    a = i0 + i1;
    c = a + i3;
end
```


Verilog – Attention !

 - Try to add “**bit length**” when write **constant**



```
assign next_pc = pc + 32'd4;
```

Verilog – Attention !

- A signal can't be updated in different always block or continuous assignment

- **Sequential**

E.g.

- when `cs == `S1`
 `a = 2`
- when `cs == `S2`
 `a = 1`
- else
 `a = 0`


```
always@(posedge clk) begin
    if (cs == `S0)
        a <= 2;
    else if (cs == `S1)
        a <= 1;
    else
        a <= 0;
end
```

- **Combinational (Method 1)**

```
always@(*) begin
    if (cs == `S1)
        a = 2;
    else if (cs == `S2)
        a = 1;
    else
        a = 0;
end
```


- **Combinational (Method 2)**
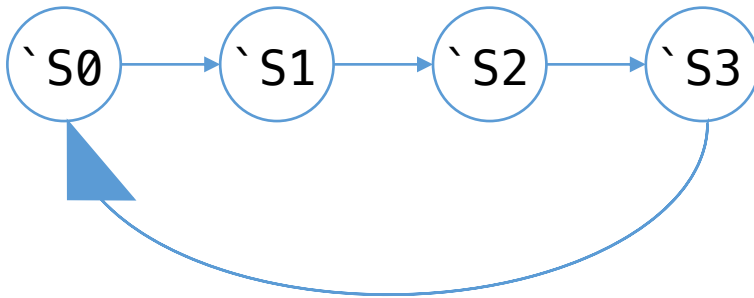
```
assign a = (cs == `S1) ? 2 :
            (cs == `S2) ? 1 : 0;
```



Verilog – Attention !

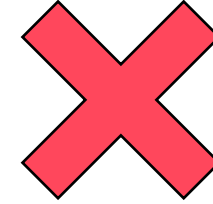- **Don't assign initial value when declaring it**
- **Combinational : No need to consider initial value**




```
wire [3:0] a = 4'b1010;  
reg [2:0] b = 3'b010;
```



output is always calculated by input

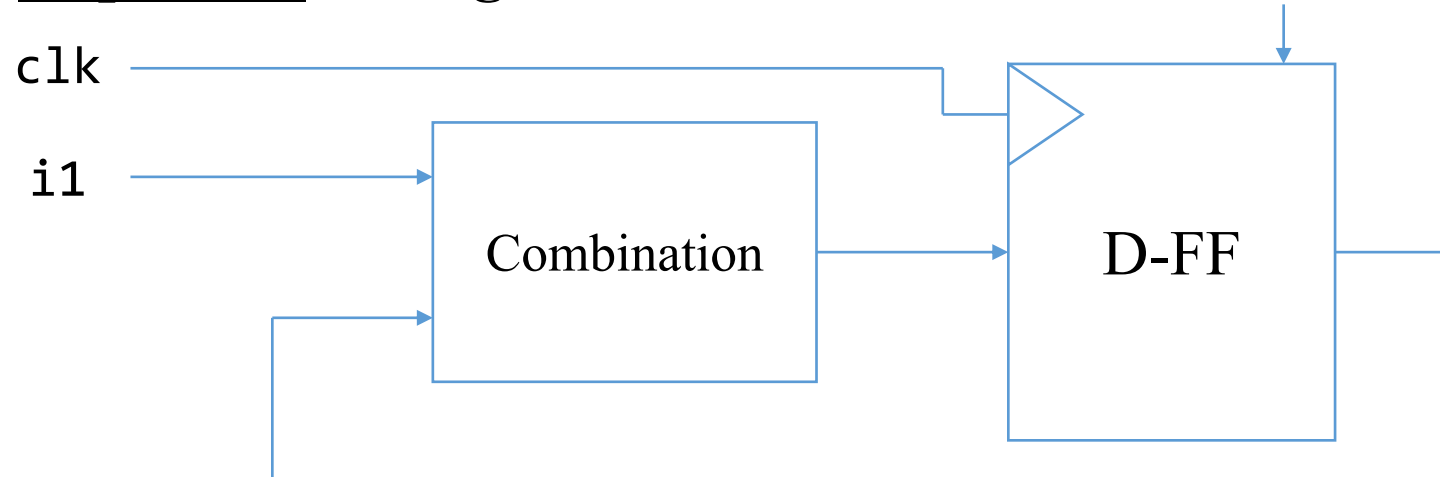- **Sequential : Assign initial value when reset**




```
always@(posedge clk) begin  
    if (rst)  
        cs <= `S0;  
    else  
        cs <= ns;  
end
```

Verilog – Attention !

- In always block, it will **implicit execute (signal = signal)**, when there is no value assigned to the signal



```
always@(posedge clk) begin
    if (rst)
        total <= 0;
    else if (cs == `S3)
        total <= 0;
end
```

total <= total;

 

```
always@(*) begin
    if (cs == `S1)
        total = input;
    else if (cs == `S3)
        total = 0;
end
```


total = total;

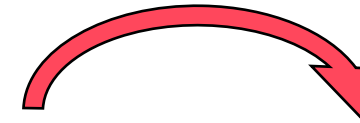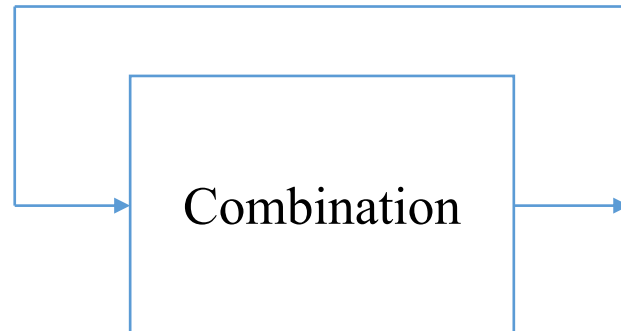

!!! Combinational need to fill up all situations !!!


```
always@(*) begin
    if (cs == `S1)
        total = input;
    else if (cs == `S3)
        total = 0;
    else
        total = 0;
end
```

total = total;
total = total + 3;

 

IC Design Level

 
二下 邱瀝毅 超大型積體電路電腦輔助設計概論
三下 張順志 VLSI 電路設計
碩博(上) 蘇培陞 SystemC 與行為階層設計
碩博(下) 蘇培陞 電子系統層級設計特論




CPU Architecture Review



How a CPU execute a program ?

 

Register & Main Memory

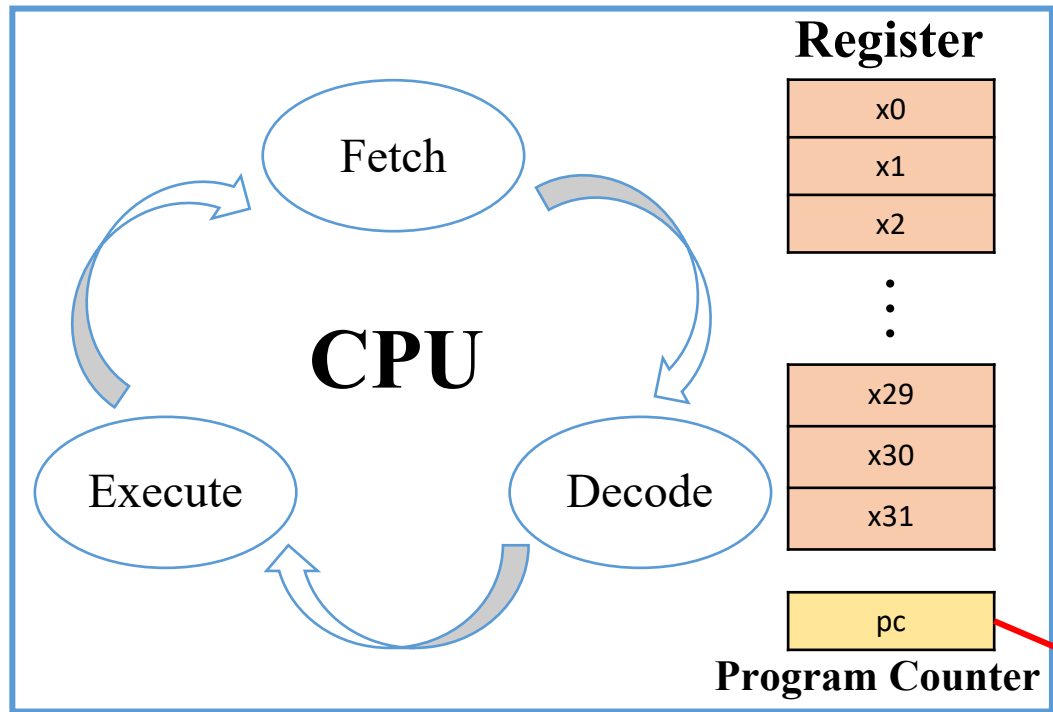


RAM

0xbfffffff0

Register is faster than RAM

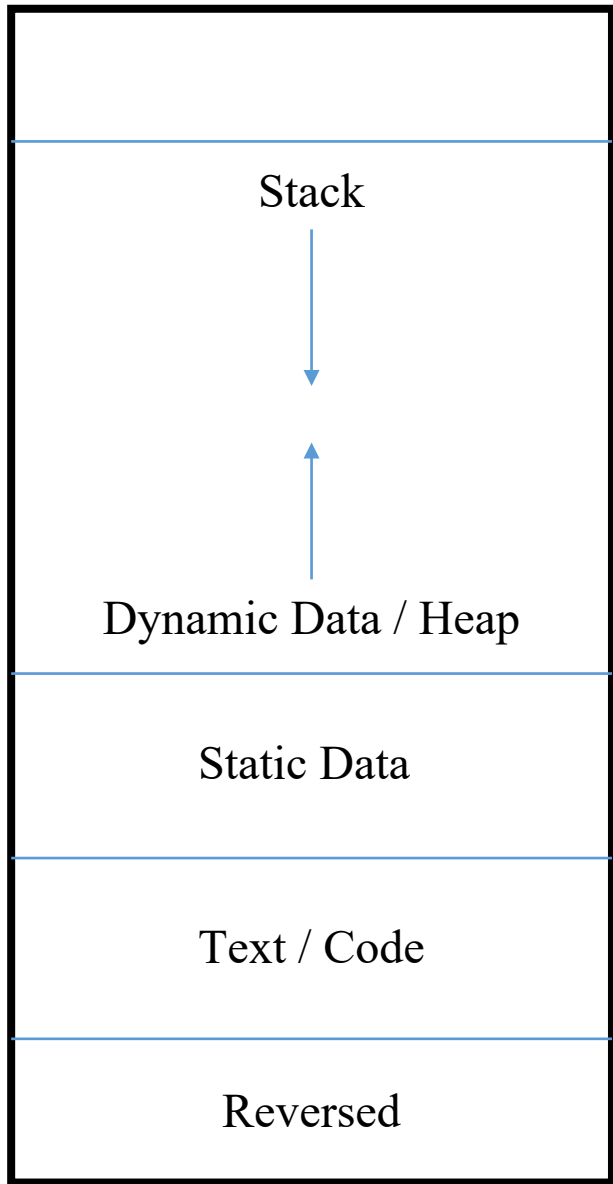So, RISC need to load data from memory to registers before computing



3 stages :

- Fetch : Fetch an **instruction that pc points to** from RAM
- Decode : Decode the fetched instruction to know what it mean
- Execute : Execute the instruction according the decode result

0x00010000


0x00000000



Example of CPU Micro-Architecture




CPU Block Diagram (Data Path)

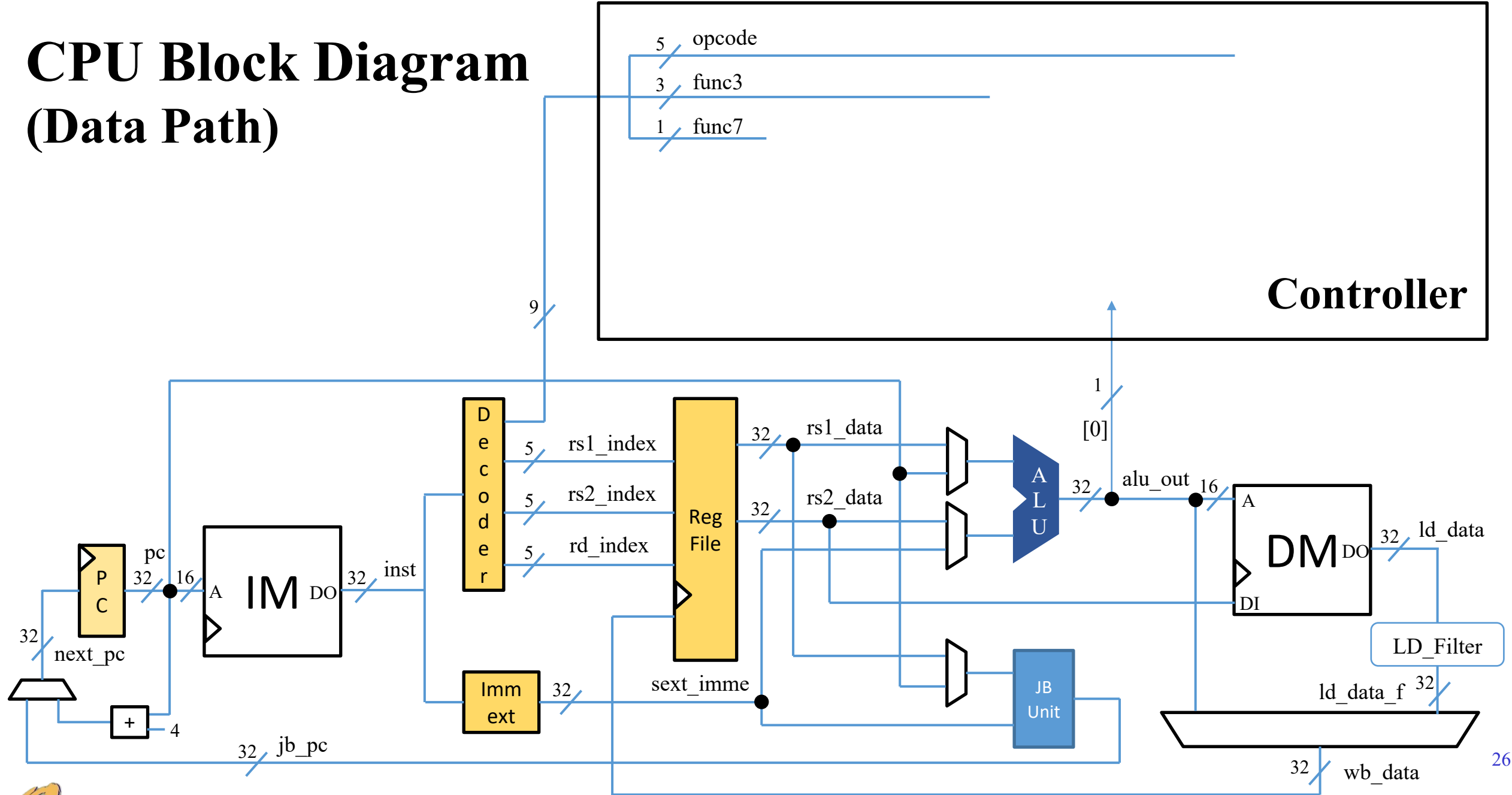

Module – SRAM


```
module SRAM (  
    input clk,  
    input [3:0] w_en,  
    input [15:0] address,  
    input [31:0] write_data,  
    output [31:0] read_data  
);  
    reg [7:0] mem [0:65535];
```

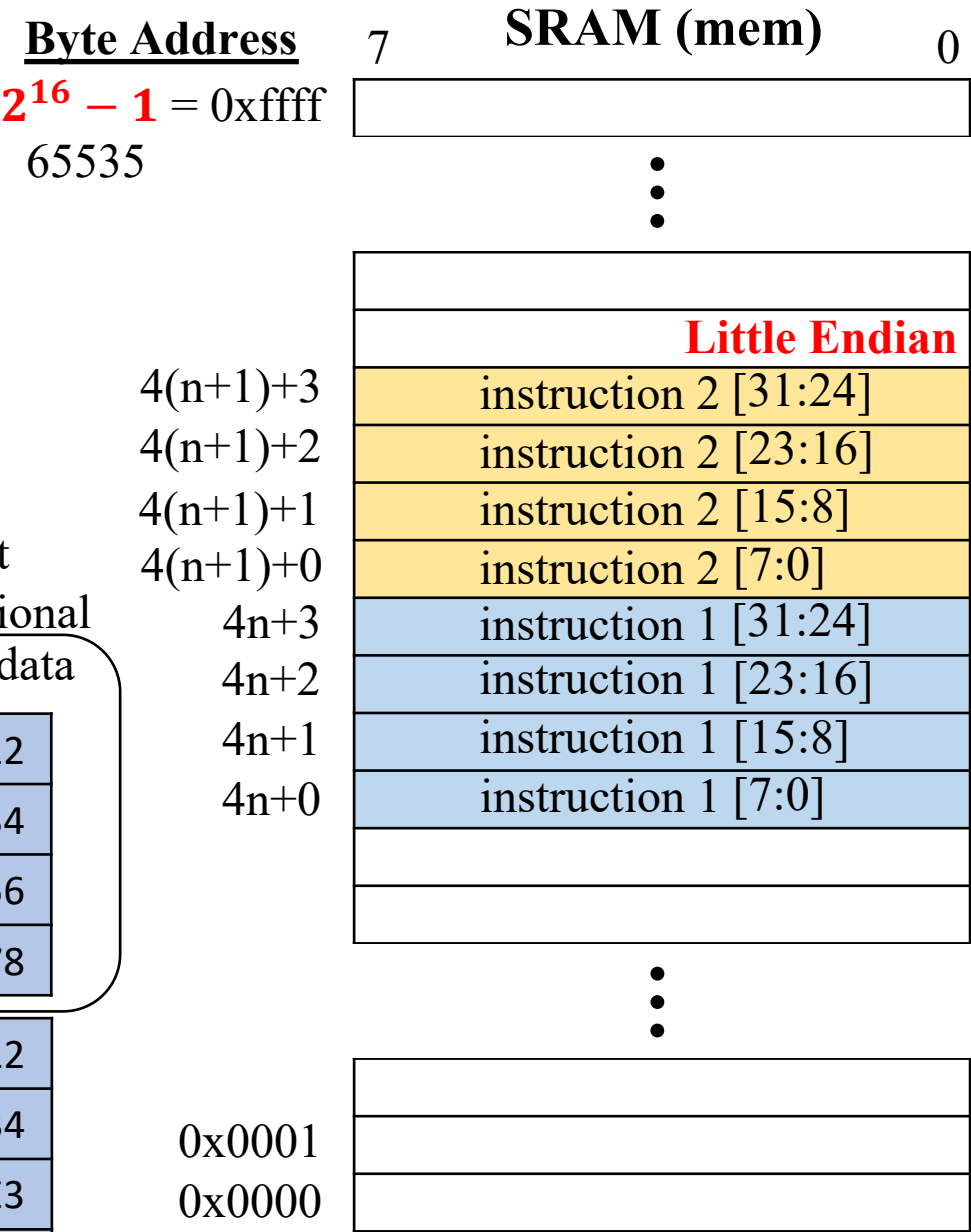E.g.
Suppose
t0 = 0xDA9BE327
t1 = 0x7
sh t0, 0(t1)
=> w_en = 4'b0011




Cycle N


Cycle N+1

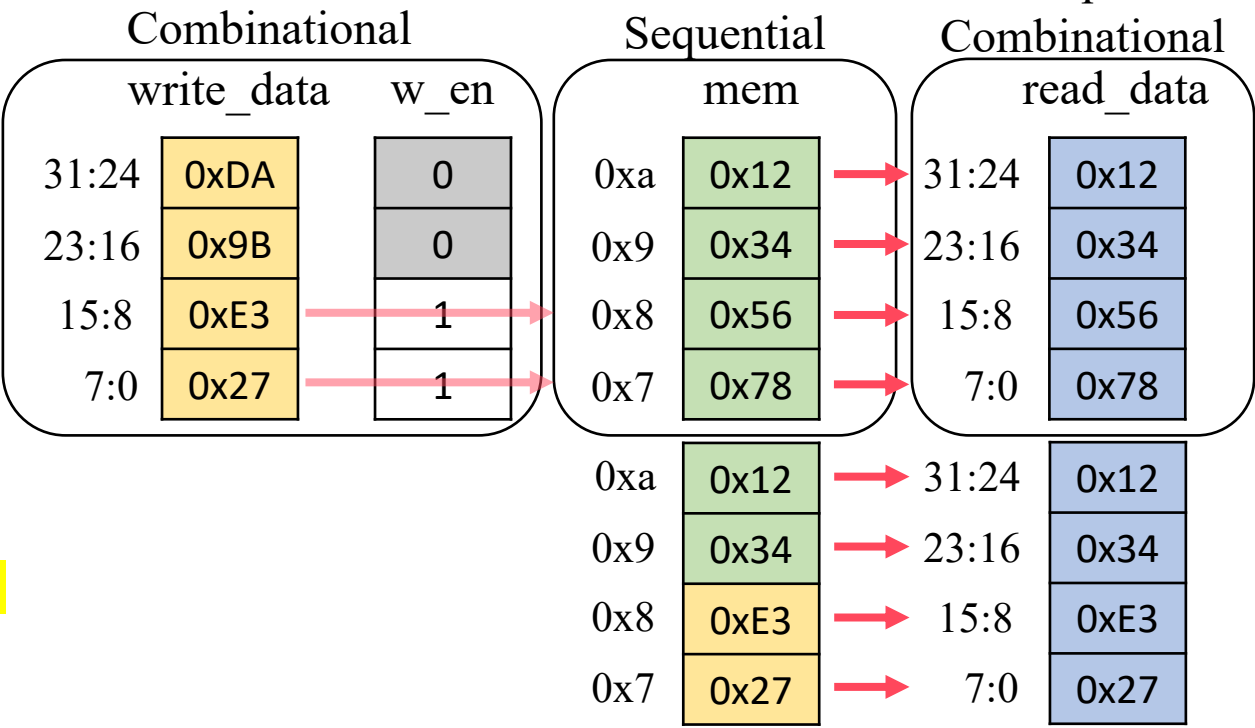

CPU Block Diagram (Data + Control Path)

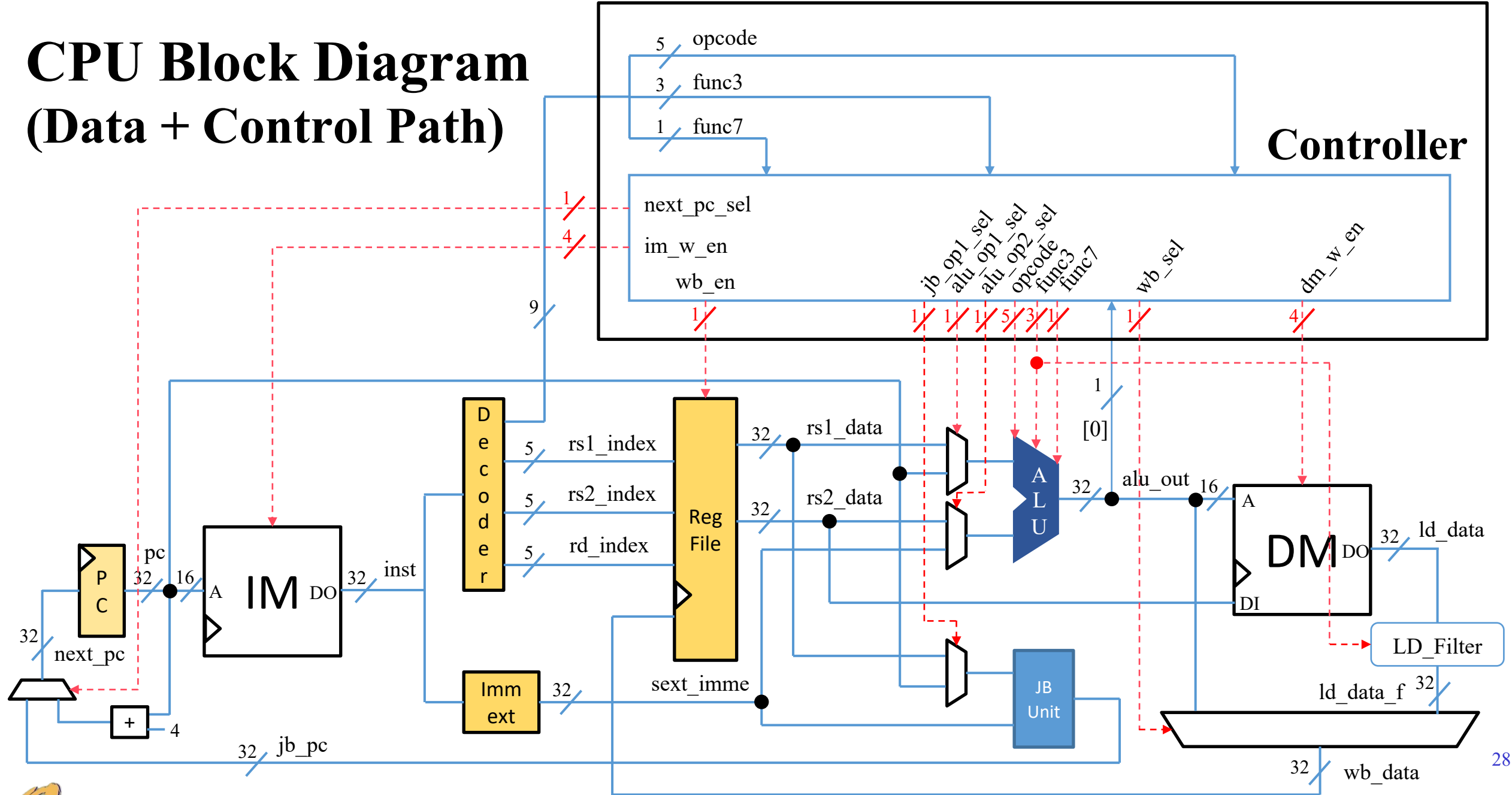

CPU Block Diagram (Data + Control Path)

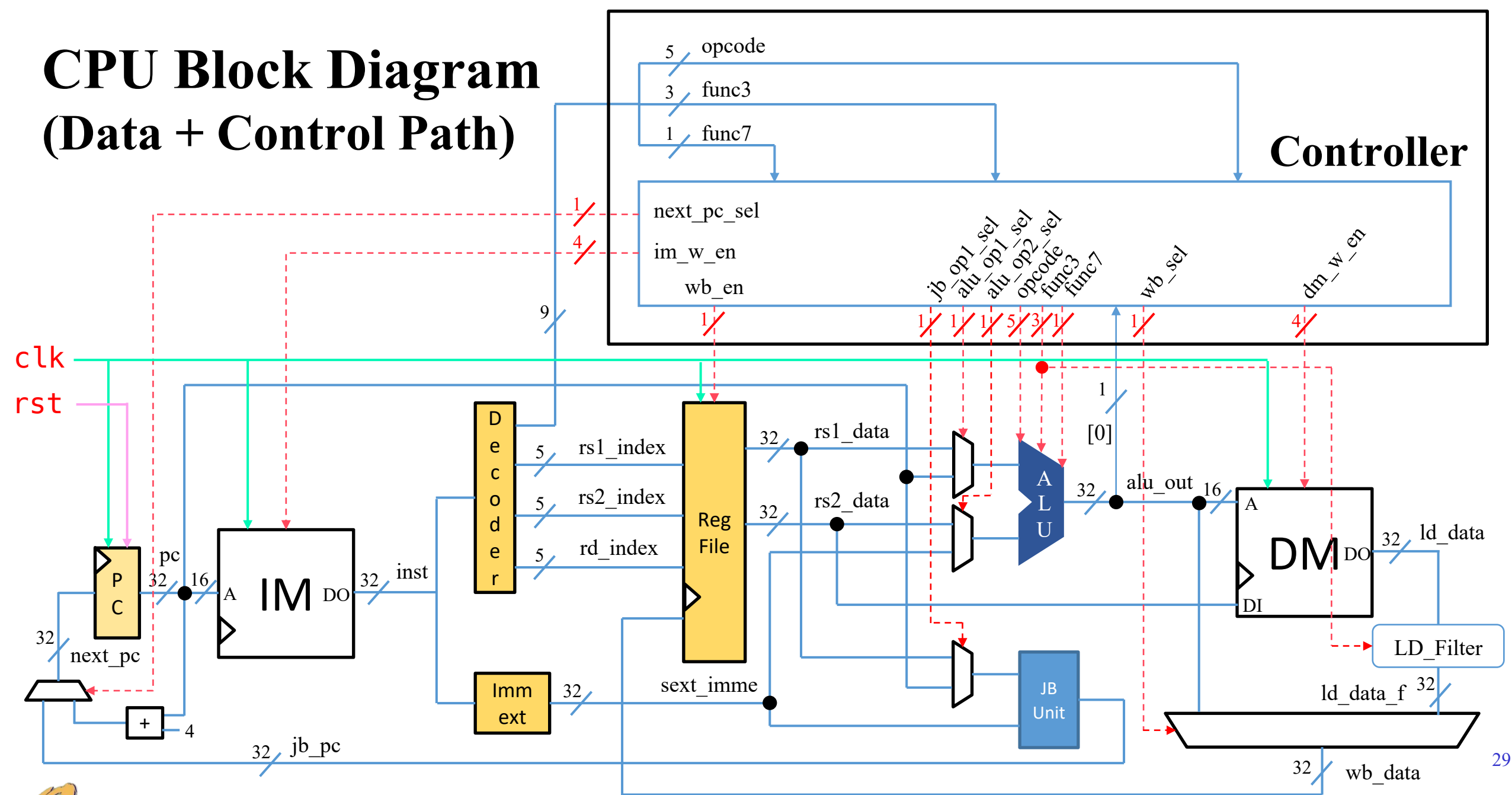


CPU Block Diagram (Data Path)


Module – Reg_PC

```
module Reg_PC (  
    input clk,  
    input rst,  
    input [31:0] next_pc,  
    output reg [31:0] current_pc  
);
```

current_pc reset from 32'd0

 

CPU Block Diagram (Data Path)

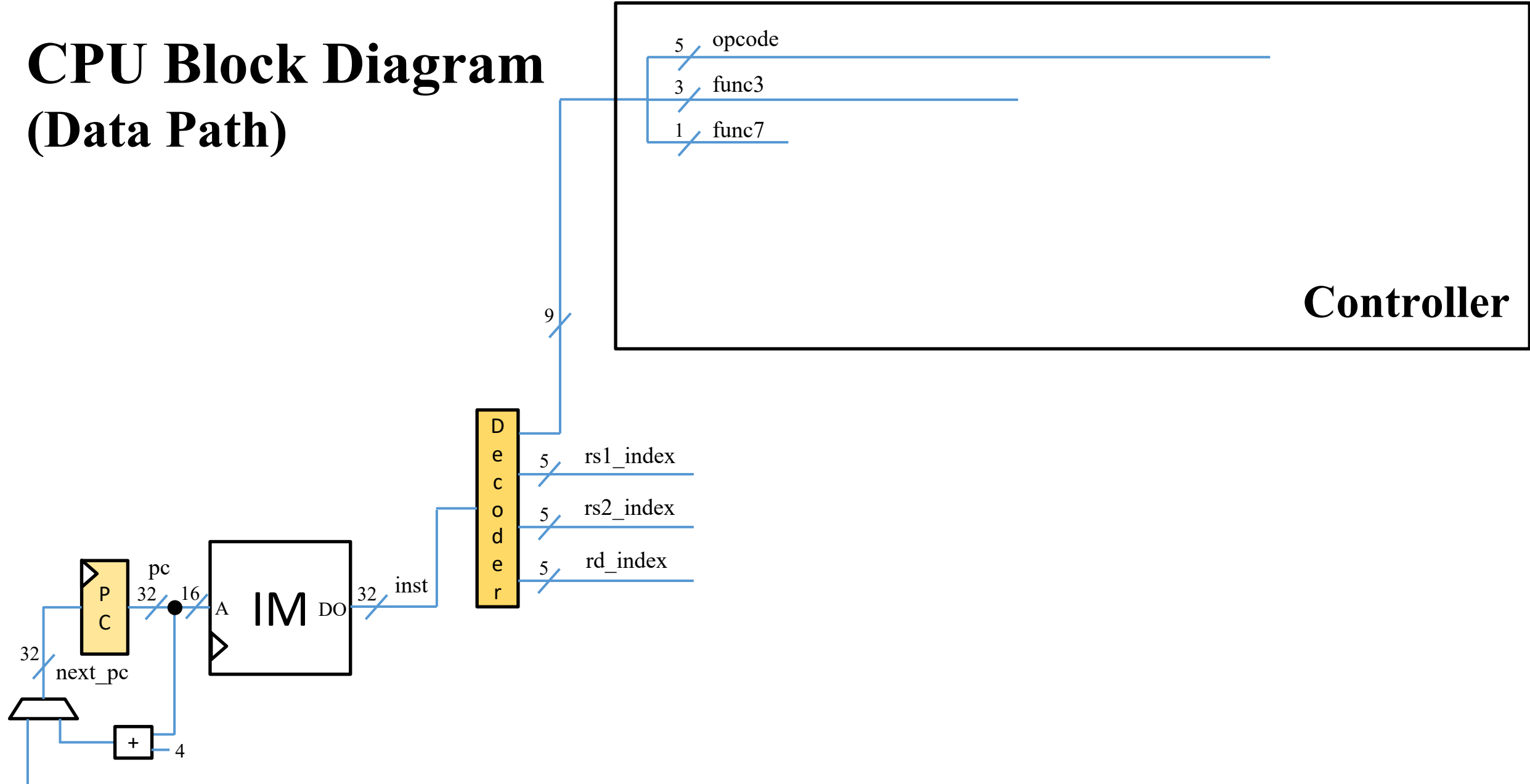

Module – Decoder

```
module Decoder (  
    input [31:0] inst,  
    output [4:0] dc_out_opcode,  
    output [2:0] dc_out_func3,  
    output      dc_out_func7,  
    output [4:0] dc_out_rs1_index,  
    output [4:0] dc_out_rs2_index,  
    output [4:0] dc_out_rd_index  
);
```

opcode : the operation of the instruction
func3 : support opcode to express the operation
func7 : support opcode to express the operation
rs1 : source register 1
rs2 : source register 2
rd : destination register

Formats	32 Bits (RV32I)																															
	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
R type	func7							rs2					rs1					func3			rd					opcode						
I type	imme[11:0]												rs1					func3			rd					opcode						
S type	imme[11:5]							rs2					rs1					func3			imme[4:0]					opcode						
B type	{ imme[12], imme[10:5] }							rs2					rs1					func3			{ imme[4:1], imme[11] }					opcode						
U type	imme[31:12]																				rd					opcode						
J type	{ imme[20], imme[10:1], imme[11], imme[19:12] }																				rd					opcode						




RISC-V - Overview of RV32I Instructions

imm[31:12]				rd	0110111	U lui
imm[31:12]				rd	0010111	U auipc
imm[20 10:1 11 19:12]				rd	1101111	J jal
imm[11:0]		rs1	000	rd	1100111	I jalr
imm[12 10:5]	rs2	rs1	000	imm[4:1 11]	1100011	B beq
imm[12 10:5]	rs2	rs1	001	imm[4:1 11]	1100011	B bne
imm[12 10:5]	rs2	rs1	100	imm[4:1 11]	1100011	B blt
imm[12 10:5]	rs2	rs1	101	imm[4:1 11]	1100011	B bge
imm[12 10:5]	rs2	rs1	110	imm[4:1 11]	1100011	B bltu
imm[12 10:5]	rs2	rs1	111	imm[4:1 11]	1100011	B bgeu
imm[11:0]		rs1	000	rd	0000011	I lb
imm[11:0]		rs1	001	rd	0000011	I lh
imm[11:0]		rs1	010	rd	0000011	I lw
imm[11:0]		rs1	100	rd	0000011	I lbu
imm[11:0]		rs1	101	rd	0000011	I lhu
imm[11:5]	rs2	rs1	000	imm[4:0]	0100011	S sb
imm[11:5]	rs2	rs1	001	imm[4:0]	0100011	S sh
imm[11:5]	rs2	rs1	010	imm[4:0]	0100011	S sw

imm[11:0]		rs1	000	rd	0010011	I addi
imm[11:0]		rs1	010	rd	0010011	I slti
imm[11:0]		rs1	011	rd	0010011	I sltiu
imm[11:0]		rs1	100	rd	0010011	I xori
imm[11:0]		rs1	110	rd	0010011	I ori
imm[11:0]		rs1	111	rd	0010011	I andi
0000000	shamt	rs1	001	rd	0010011	I slli
0000000	shamt	rs1	101	rd	0010011	I srli
0100000	shamt	rs1	101	rd	0010011	I srai
0000000	rs2	rs1	000	rd	0110011	R add
0100000	rs2	rs1	000	rd	0110011	R sub
0000000	rs2	rs1	001	rd	0110011	R sll
0000000	rs2	rs1	010	rd	0110011	R slt
0000000	rs2	rs1	011	rd	0110011	R sltu
0000000	rs2	rs1	100	rd	0110011	R xor
0000000	rs2	rs1	101	rd	0110011	R srl
0100000	rs2	rs1	101	rd	0110011	R sra
0000000	rs2	rs1	110	rd	0110011	R or
0000000	rs2	rs1	111	rd	0110011	R and

Decode – Ignore last 2 bits

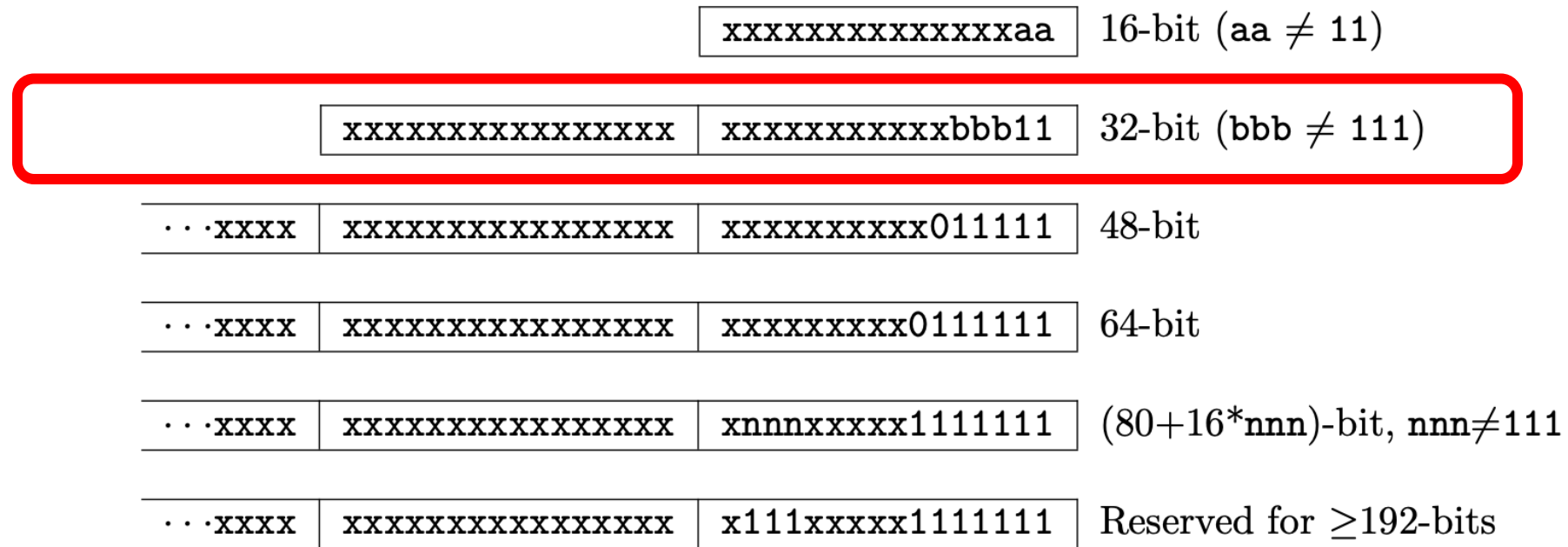- Instruction Length of Base ISA are all 32 bits
- If Including Compressed Extension ISA Instruction Length can be 16 bits or 32 bits
- Decoder will use the last n bits to determine which length it is
- **In this lab, we only consider RV32I (base ISA), so the last 2 bits are always 11**




Byte Address: base+4

base+2

base

CPU Block Diagram (Data Path)

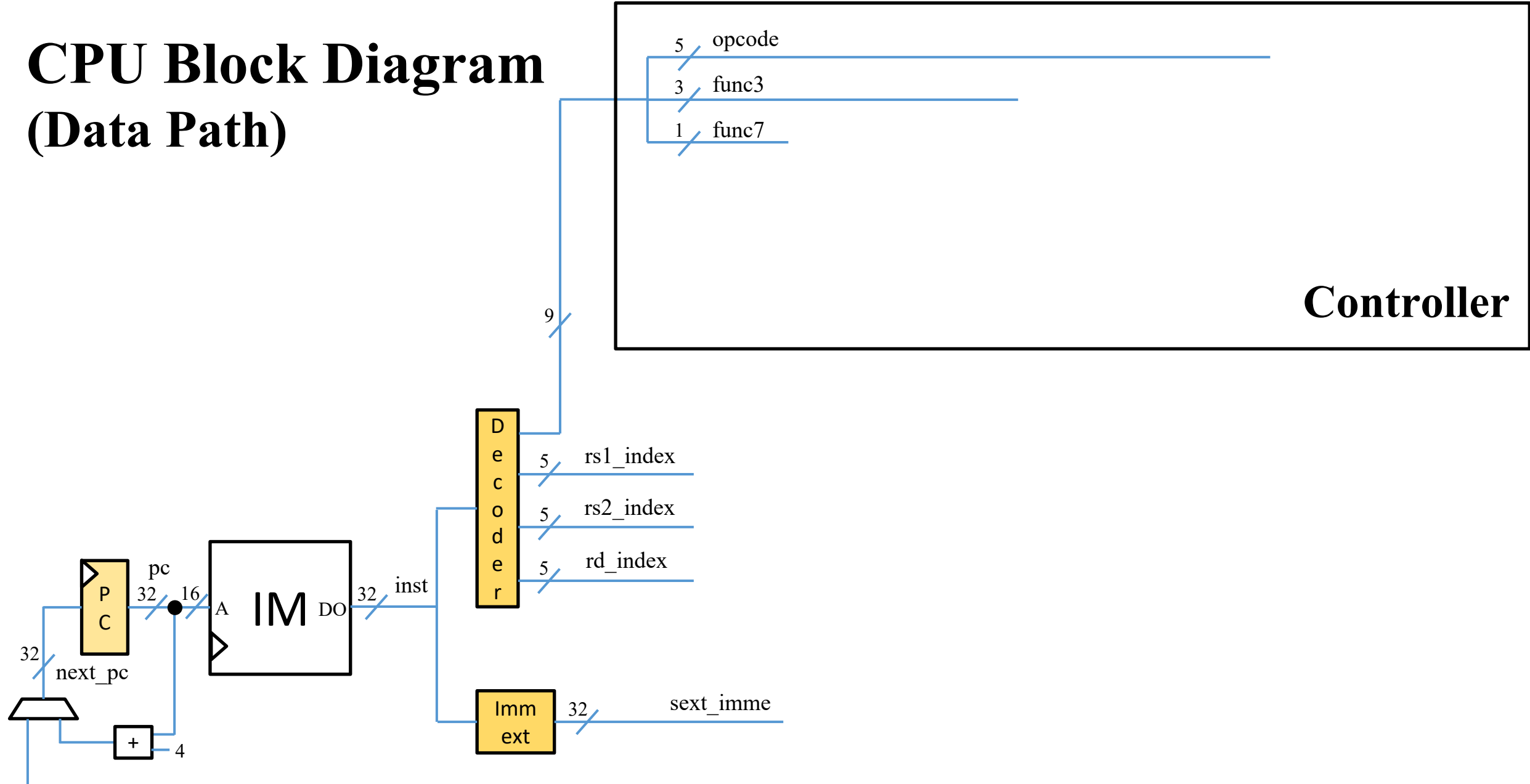


Module – Imm_Ext

```
module Imm_Ext (
    input [31:0] inst,
    output [31:0] imm_ext_out
);
```

Type	imm_ext_out
R type	–
I type	{{20{inst[31]}}, inst[31: 20]}
S type	{{20{inst[31]}}, inst[31: 25], inst[11: 7]}
B type	{{20{inst[31]}}, inst[7], inst[30: 25], inst[11: 8], 1'b0}
U type	{inst[31: 12], 12'b0}
J type	{{12{inst[31]}}, inst[19: 12], inst[20], inst[30: 21], 1'b0}

Formats	32 Bits (RV32I)																															
	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
R type	func7							rs2					rs1					func3			rd					opcode						
I type	imme[11:0]												rs1					func3			rd					opcode						
S type	imme[11:5]							rs2					rs1					func3			imme[4:0]					opcode						
B type	{ imme[12], imme[10:5] }							rs2					rs1					func3			{ imme[4:1], imme[11] }					opcode						
U type	imme[31:12]																				rd					opcode						
J type	{ imme[20], imme[10:1], imme[11], imme[19:12] }																				rd					opcode						


CPU Block Diagram (Data Path)

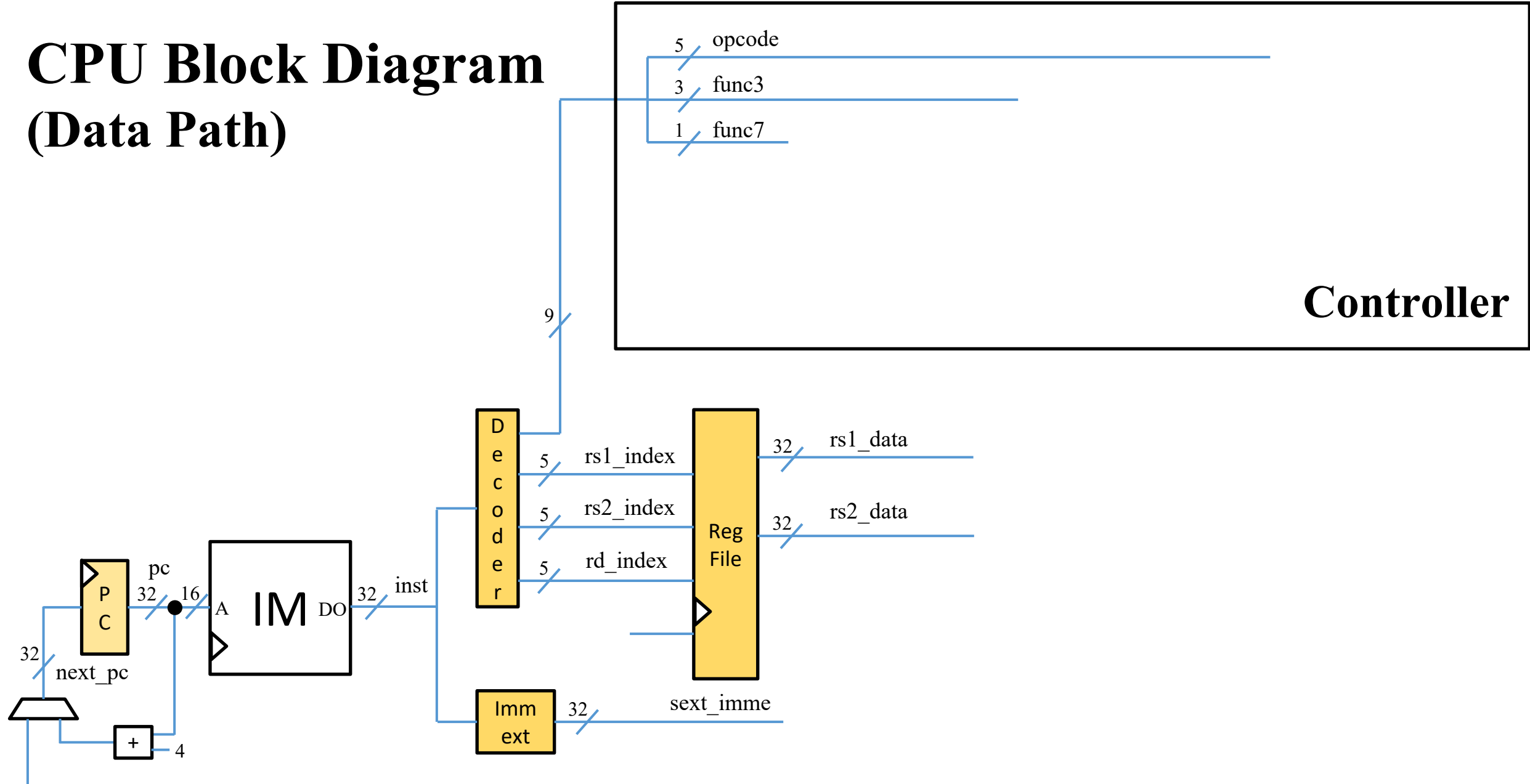

Module – RegFile


```
module RegFile (
    input clk,
    input wb_en,
    input [31:0] wb_data,
    input [4:0] rd_index,
    input [4:0] rs1_index,
    input [4:0] rs2_index,
    output [31:0] rs1_data_out,
    output [31:0] rs2_data_out
);
    reg [31:0] registers [0:31];
```

Cycle N

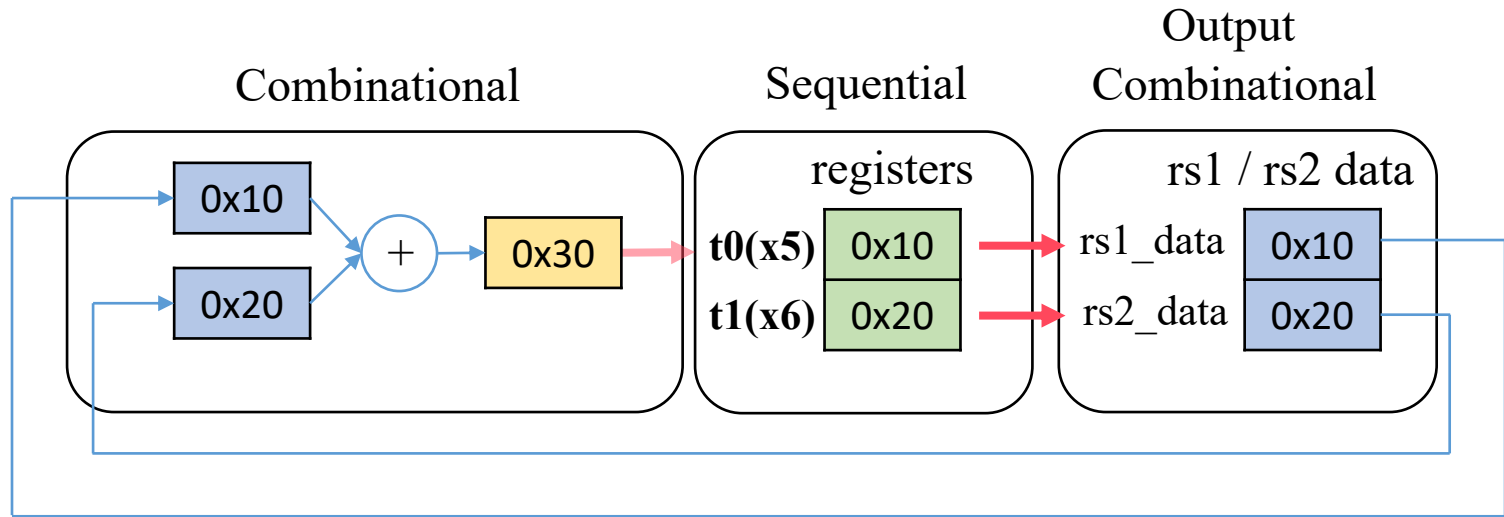

Cycle N+1

sxt(imm)

 

E.g.

Suppose

t0 = 0x10

t1 = 0x20


s0 = 0x11

add t0, t0, t1 => wb_en = 1'b1

addi t1, t0, 40 => wb_en = 1'b1

addi t1, t0, 40 : 0000001**01000** 00101 000 00110 0010011

CPU Block Diagram (Data Path)

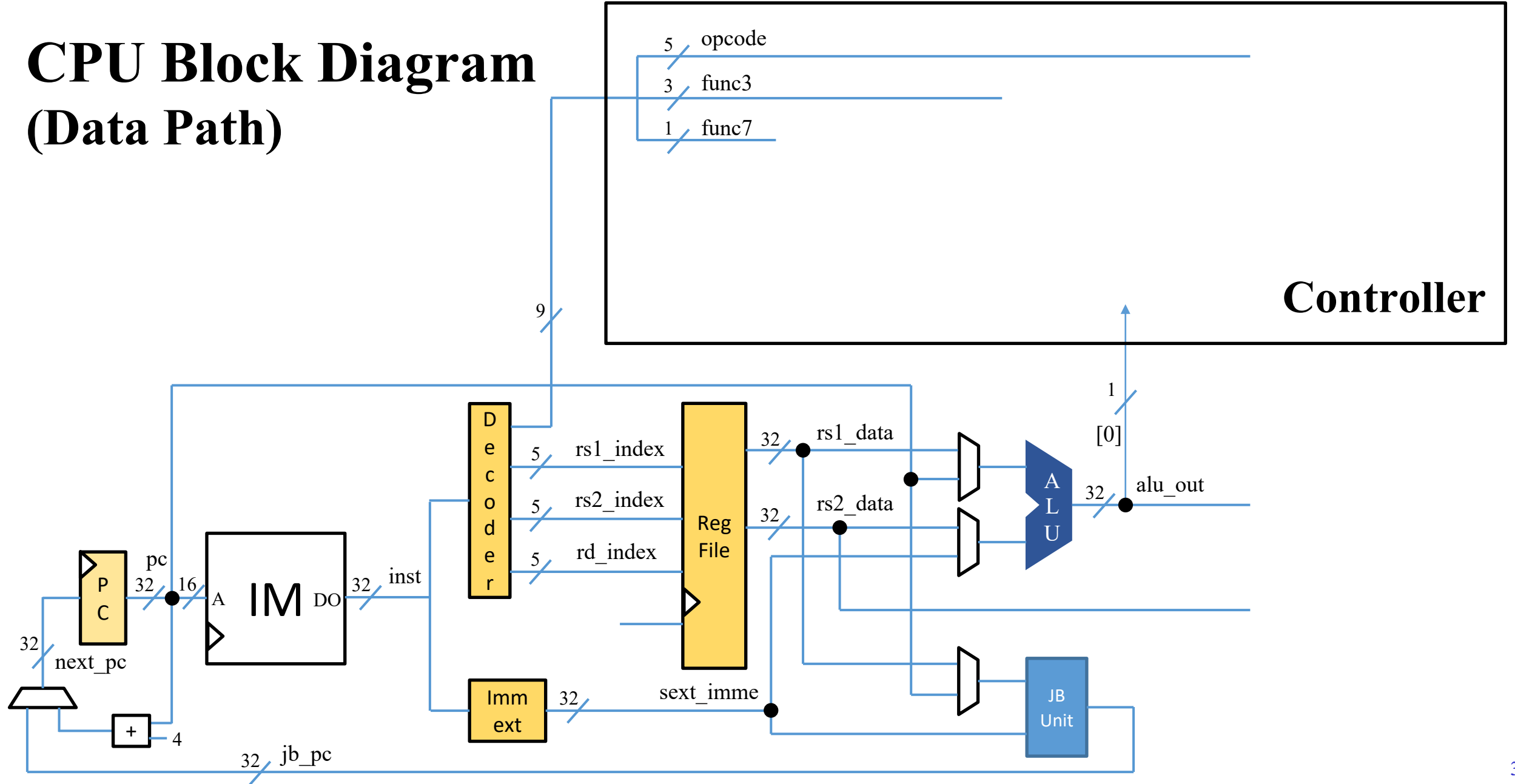

Instruction classification of RV32I depends on functionality

- Computation Instruction

- Register – Register
- Register – Immediate
- Long Immediate

Arithmetic Set Shift Logical

(add, **sub**, **slt**, **sltu**, sll, srl, sra, **xor**, or, and)
(addi, **slti**, **sltiu**, slli, srli, srai, **xori**, ori, andi)
(lui, auipc)

- Load & Store Instruction

- Load
- Store

(lb, lh, lw, lbu, lhu)
(sb, sh, sw)

- Control Transfer Instruction

- Unconditional Jump
- Conditional Branch

(jal, jalr)
(beq, bne, blt, bge, bltu, bgeu)



Instruction classification of RV32I depends on functionality

	ALU operation	alu_op1	alu_op2	JB_Unit operation	jb_unit_op1	jb_unit_op2
Computation Instruction						
Register - Register	rs1 interacts with rs2	rs1	rs2	–	–	–
Register - Immediate	rs1 interacts with imm	rs1	imm	–	–	–
LUI	imm	–	imm	–	–	–
AUIPC	pc + imm	pc	imm	–	–	–
Load & Store Instruction						
Load	rs1 + imm => calculate address	rs1	imm	–	–	–
Store	rs1 + imm => calculate address	rs1	imm	–	–	–
Control Transfer Instruction						
JAL	pc + 4	pc	–	pc + imm	pc	imm
JALR	pc + 4	pc	–	(rs1 + imm) & (~32'd1)	rs1	imm
Branch	rs1 compares with rs2	rs1	rs2	pc + imm	pc	imm


Module – ALU / JB_Unit

```
module ALU (
    input [4:0] opcode,
    input [2:0] func3,
    input      func7,
    input [31:0] operand1,
    input [31:0] operand2,
    output [31:0] alu_out
);
```

```
module JB_Unit (
    input [31:0] operand1,
    input [31:0] operand2,
    output [31:0] jb_out
);
```

	ALU operation	JB_Unit operation
Computation Instruction		
Register - Register	$op1 \xleftrightarrow{(f3,f7)} op2$	–
Register - Immediate	$op1 \xleftrightarrow{(f3,f7)} op2$	–
LUI	$op2$	–
AUIPC	$op1 + op2$	–
Load & Store Instruction		
Load	$op1 + op2 \Rightarrow \text{address}$	–
Store	$op1 + op2 \Rightarrow \text{address}$	–
Control Transfer Instruction		
JAL	$op1 + 4 \Rightarrow \text{pc} + 4$	$op1 + op2$
JALR	$op1 + 4 \Rightarrow \text{pc} + 4$	$(op1 + op2) \& (\sim 32'd1)$
Branch	$op1 \xleftrightarrow{(f3)} op2$	$op1 + op2$

CPU Block Diagram (Data Path)

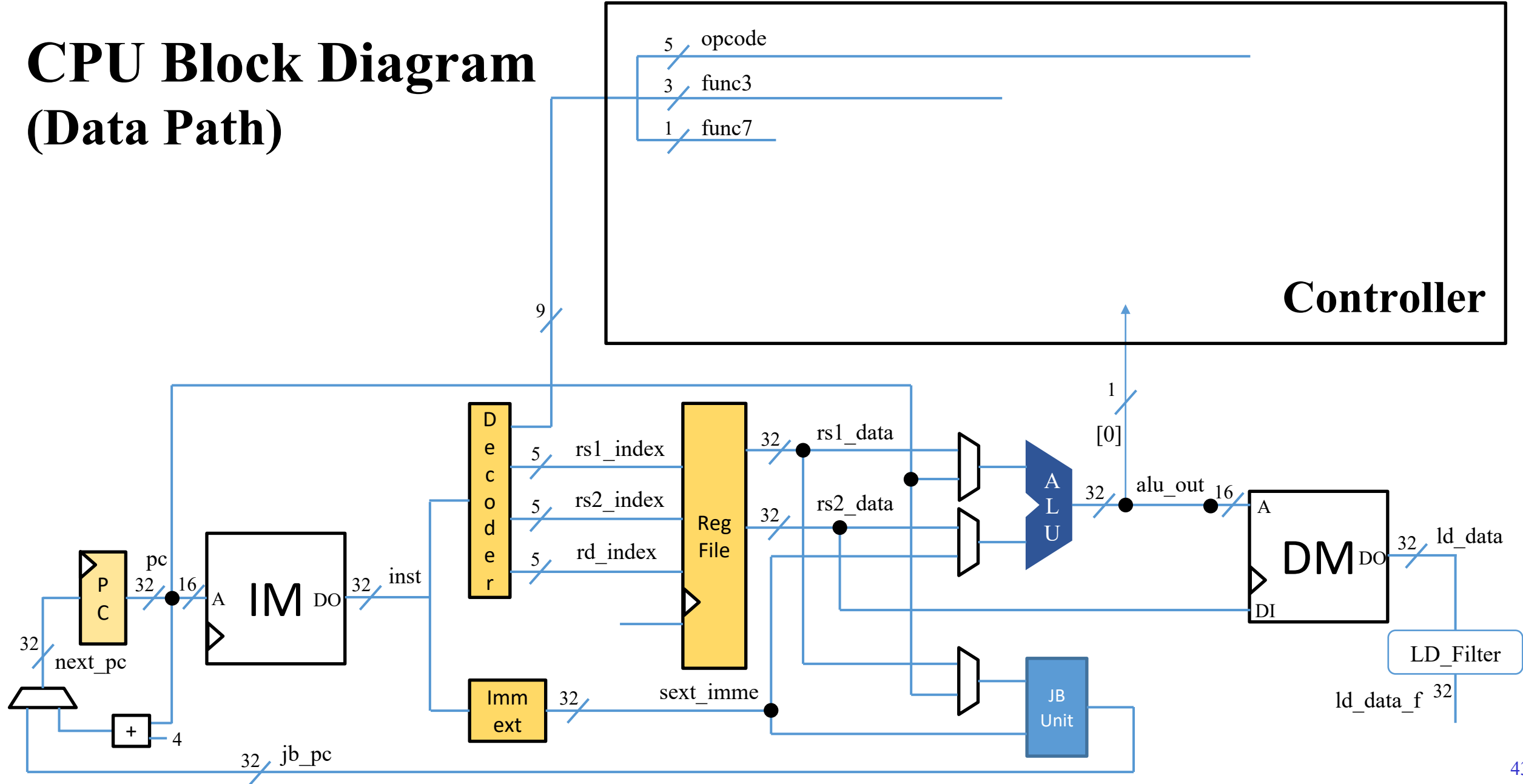

Module – LD_Filter

```

module LD_Filter (
    input [2:0] func3,
    input [31:0] ld_data,
    output [31:0] ld_data_f
);

```

func3


imm[11:0]	rs1	000	rd	0000011	I lb
imm[11:0]	rs1	001	rd	0000011	I lh
imm[11:0]	rs1	010	rd	0000011	I lw
imm[11:0]	rs1	100	rd	0000011	I lbu
imm[11:0]	rs1	101	rd	0000011	I lhu

E.g.


	32 Bits																															
	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
ld_data	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0
lb	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	<u>1</u>	0	1	0	1	0	1	0
lbu	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	0	1	0	1	0




CPU Block Diagram (Data Path)

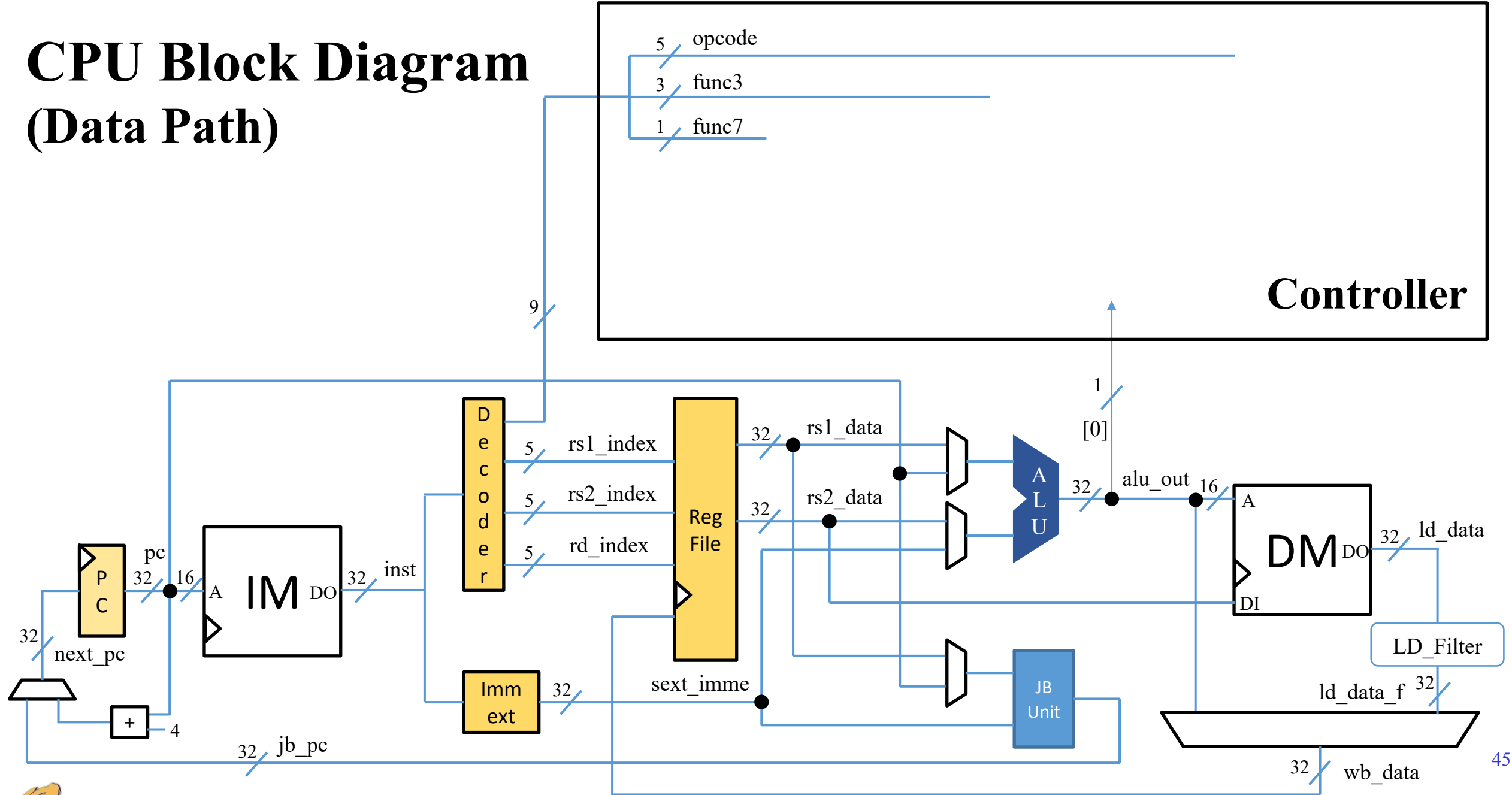

CPU Block Diagram (Data + Control Path)

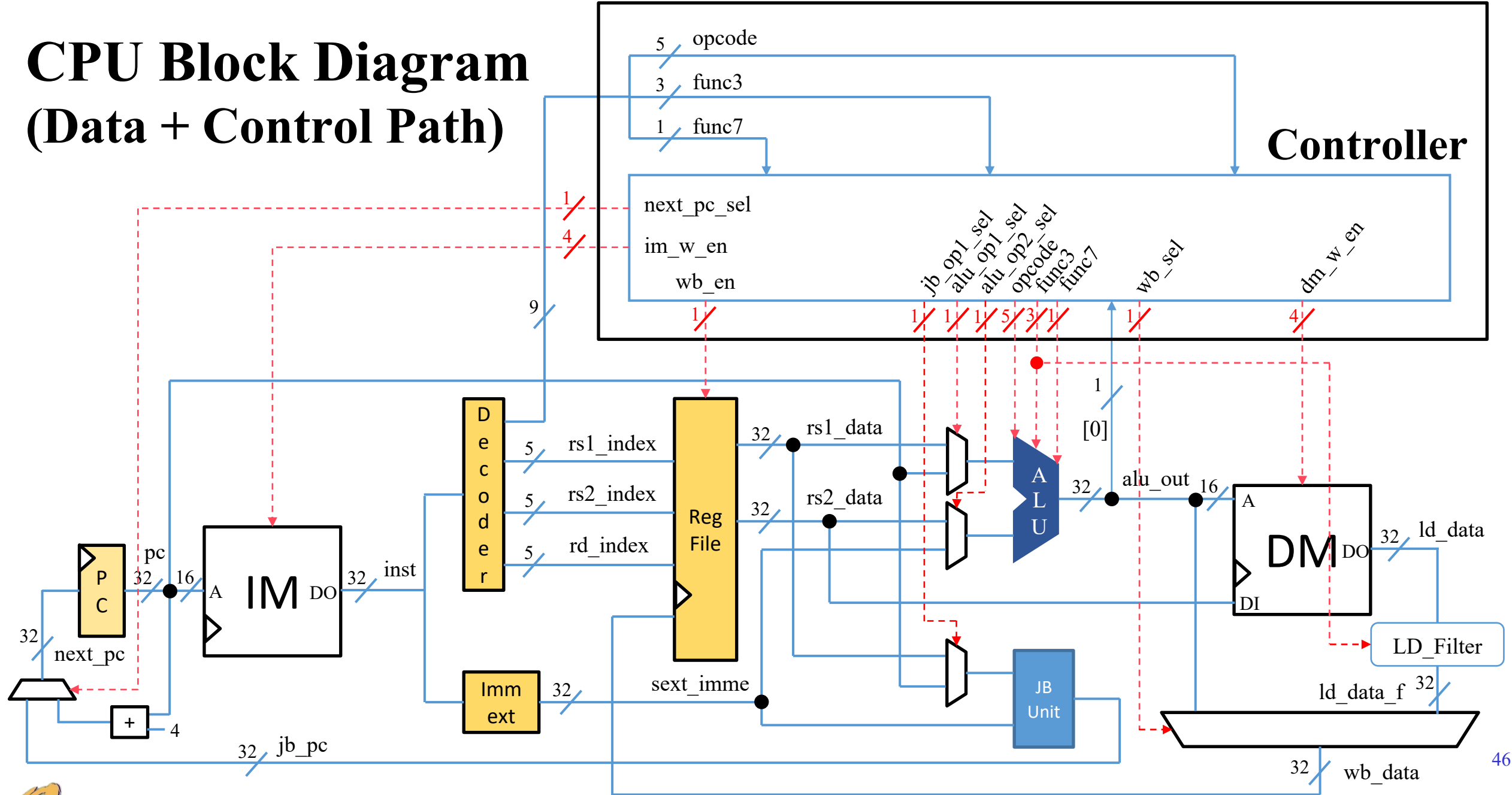

CPU Block Diagram (Data + Control Path)

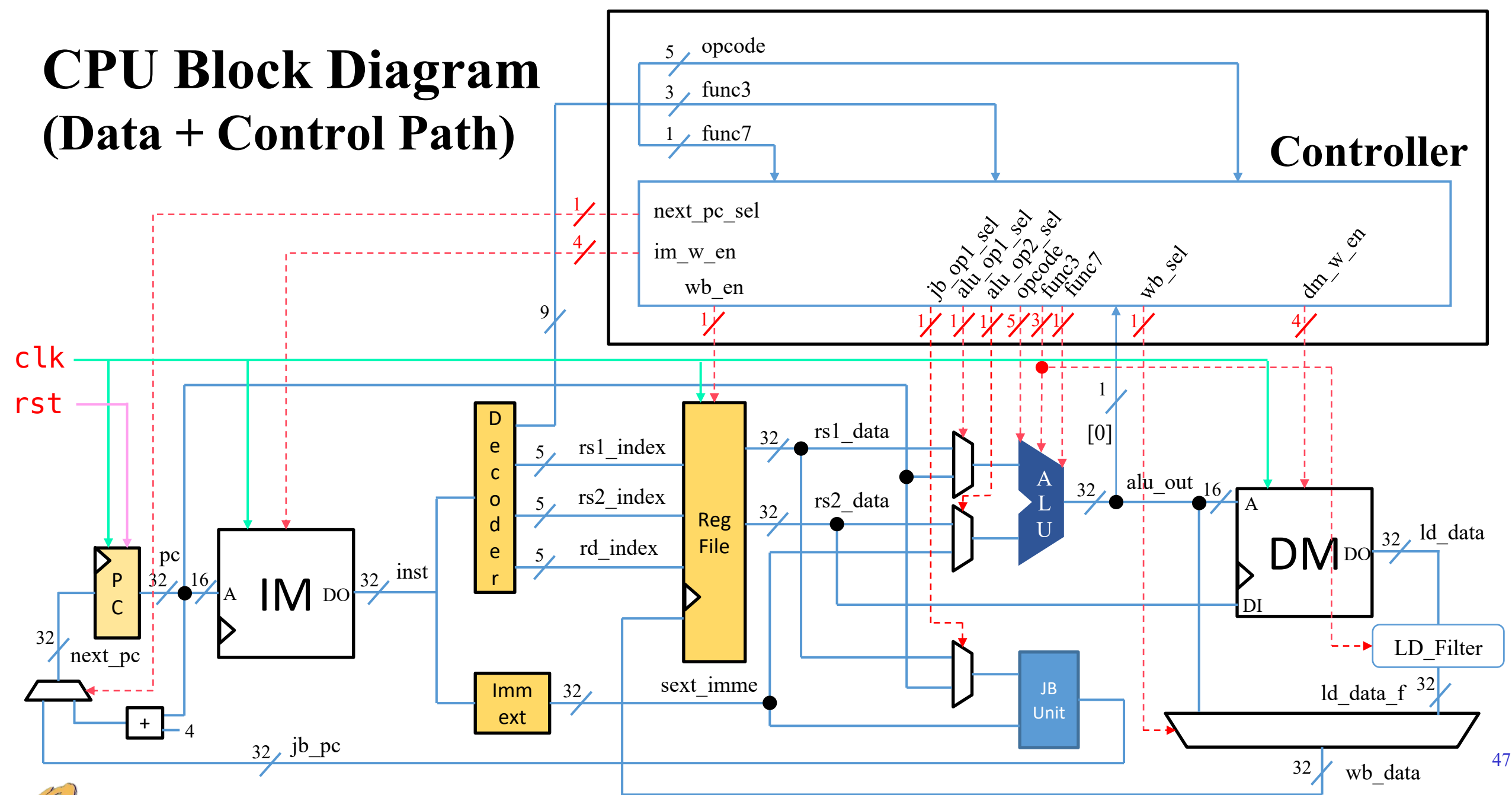


Module List

- Top.v
 - ALU.v
 - Decoder.v
 - Imme_Ext.v
 - JB_Unit.v
 - LD_Filter.v
 - RegFile.v
 - Adder.v
 - Reg_PC.v
 - Mux.v
 - SRAM.v
 - Controller.v

```
module Top (  
    input clk,  
    input rst  
);  
    SRAM im(  
        ...  
    );  
    SRAM dm(  
        ...  
    );  
    ...  
endmodule
```

current_pc reset from 32'd0

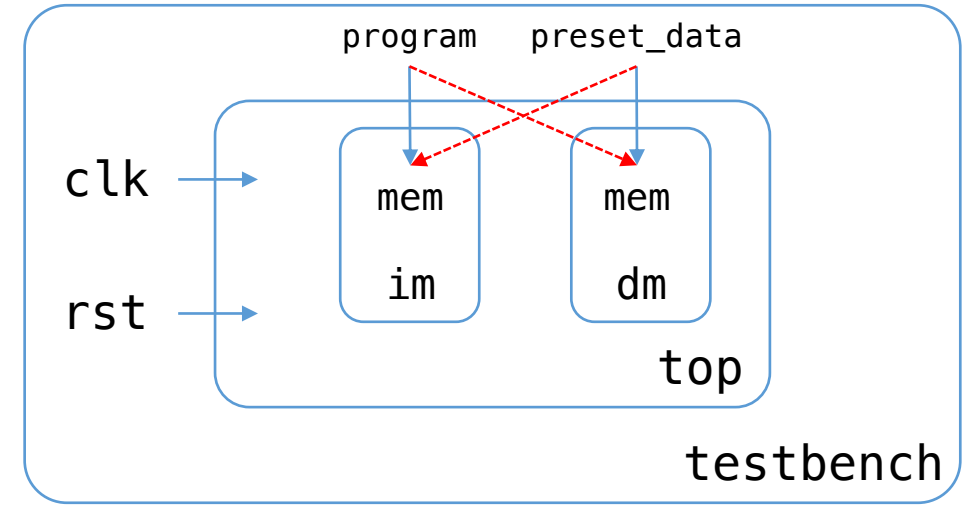

- You can use reg on output when you need it
- Try to separate different modules in different files
- Finally, instance all of the modules and connect them in the Top module.